

EXPERIMENT NUMBER 7

Properties of the Operational Amplifier

Preface:

- **Preliminary** exercises are to be done and submitted individually and turned in **at the beginning of class**
- Laboratory hardware exercises are to be done in groups
- The **Lab Report** is the **Lab Notebook**, and it can be written by any one member of the group
- The student-group **MUST** have the data and answers acquired during the lab and entered in the **Lab Notebook** verified by the TA before they leave the class
- Failure to show the **Lab Notebook** to the TA, will result in no score for **Lab Report** for the entire group
- **Tech Memo** to be done in Word Doc according to the format uploaded on CANVAS and submitted by individual students at the **beginning of the next class**
- Review the guidelines for plagiarism to be aware of acceptable laboratory and classroom practices.

Operational amplifiers, or Op Amps, are versatile elements in many amplifier circuits. This laboratory explores the characteristics of Op Amps and their use in basic amplifier configurations.

Objectives:

- To observe the characteristics of an Op Amp
- To learn how to construct a buffer, inverting, and non-inverting amplifier circuit

References:

- EE 121 Handouts.
- Cunningham, David R. and Stuller, John A., *Circuit Analysis*, 2nd ed., (John Wiley & Sons, Inc., Chichester, New York, 1995) Chapter 6.

Background:

An operational amplifier, or Op Amp, is an electronic device composed of various internal circuit components (e.g. transistors, capacitors, and resistors). It has two input terminals, two power terminals, and one output terminal. The input resistance between the two input terminals is large (ideally infinite), and thus negligible current flows into the Op Amp. The output terminal acts as a dependent voltage source with small (ideally zero) output resistance. Constant power must be supplied to the Op Amp to power it on. An example of an Op Amp chip is shown in Figure 1(a).

The input terminals of the Op Amp are the (+) terminal, or non-inverting, and the (-) terminal, or inverting. A positive voltage between the (+) and (-) terminals produce a positive voltage at the output and a negative voltage between the (+) and (-) terminals produce a negative voltage at the output. The output voltage is an amplified version of the input difference voltage. Note that an output of zero results for a voltage difference of zero. However, the gain is large such that a small input difference can produce a large output

voltage magnitude. The effective gain of an Op Amp circuit typically depends on a feedback arrangement. A connect from the output terminal back to the (-) terminal provides negative feedback and quickly the circuit reaches a stable operating point. (If positive feedback in used, the Op Amp can produce oscillations, overloads, etc.) Consider the buffer circuit in Figure 1(b). As a positive input v_s increases, the output increases and the difference between the (+) and (-) terminals is reduced. As the input v_s decreases, the output decreases and the difference between the (+) and (-) terminals is again reduced. The output v_o is drive to match the input v_s . Hence, the feedback causes allows the output to drive the input voltage difference to zero and a stable operating point reached.

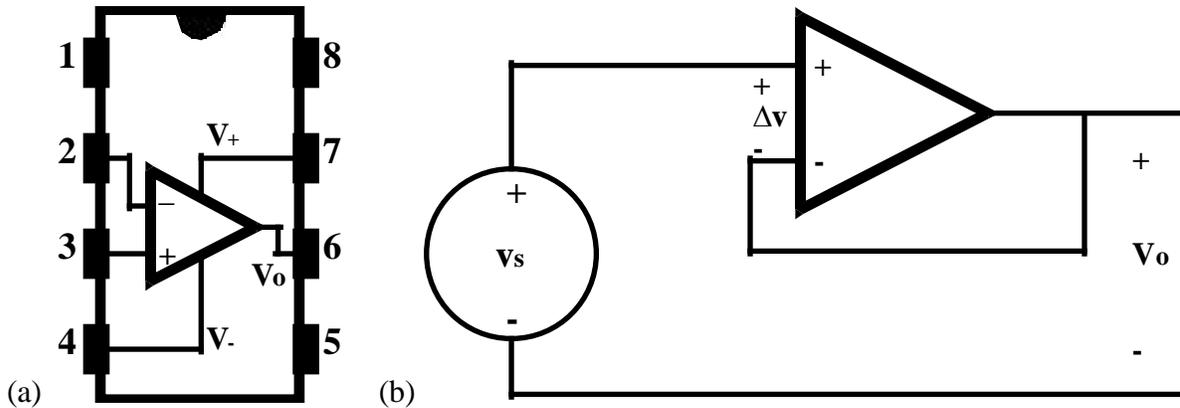


Figure 1 – (a) Op Amp Chip and (b) Buffer Op Amp Circuit

Other common Op Amp circuits are non-inverting and inverting configurations, see Figure2 and Figure 3. (A resistor is sometime placed between the (+) terminal and the reference for the circuit in Figure 3.) Circuit analysis shows the effective gains as shown.

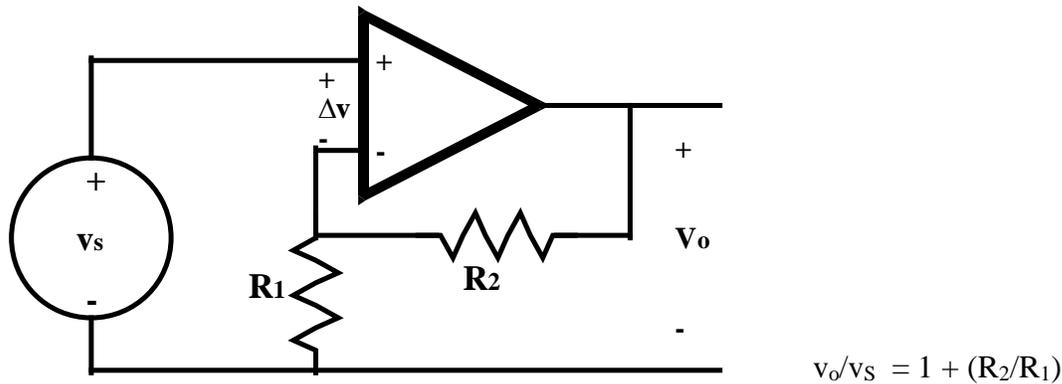


Figure 2 – Non-Inverting Op Amp Circuit

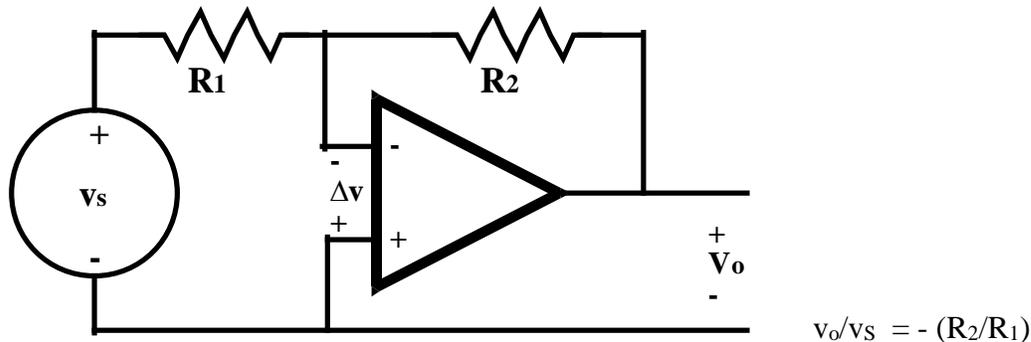


Figure 3 – Inverting Op Amp Circuit

Preliminary:

(Work on separate paper and turn in at the beginning of the laboratory session.)

- Print the data sheets for a LM741 Op Amp. Using these data sheets, identify the value of the voltage gain, maximum positive output voltage, and minimum negative output voltage.
- Consider the non-inverting Op Amp circuit in the Background. Let the (+) terminal be V_1 , the (-) terminal be V_2 , and the output be V_3 . If the Op Amp is modeled with $R_{in} = \infty$, $R_{out} = 0$, and dependent-source gain of A , (a) determine the node-voltage equations (express in matrix form). Assume that the currents into the (+) and (-) terminal are zero. (b) Determine the determinant Δ of the \mathbf{a} matrix. (c) Find V_3 using Cramer's rule or Mesh Theory (your choice). (d) Determine V_3/V_{in} as A goes to infinity.

Equipment:

- Op Amp LM741 Chip
- DC Power Supply
- DMM
- Resistors (1 k Ω , 2 k Ω , and 5 k Ω)
- Breadboard
- Oscilloscope
- Function Generator

Experimental Procedure:

(Record specifics in the Laboratory Notebook.)

1. Build the buffer Op Amp circuit with $V_{CC} = 5$ V centered at 2.5 V or greater. Connect the function generator to the input with a sine wave of 1 V peak-to-peak and 1.0 kHz. Observe the output voltage with the oscilloscope and plot or sketch the output voltage. Increase the input voltage amplitude until the output voltage curve is no longer a sine wave. Record the input voltage magnitude and the maximum and minimum output voltage values. Measure the input current by adding a resistor $R_{input} = 1$ k Ω between the function generator and the Op Amp input. Measure the voltage across the resistor and calculate the input current.

Q1: Does the circuit operation match the theoretical expectations? What limits the output magnitude?

2. Build the non-inverting Op Amp circuit with $V_{CC} = 5$ V centered at 2.5 V or greater, resistor $R_1 = 1$ k Ω (between the (-) terminal and the reference), and resistor $R_2 = 3.3$ k Ω (between the (-) terminal and the output). Connect the function generator to the input with a square wave of 1 V peak-to-peak and 1.0 kHz. Observe the output voltage with the oscilloscope, record the peak-to-peak output voltage, and plot or sketch the output voltage curve. Calculate the percent difference between the actual peak-to-peak output voltage and the theoretical voltage value. Place a load resistor $R_L = 4.7$ k Ω between the output and the reference and observe the output voltage again.

Q2: Does the circuit operation match the theoretical expectations, i.e. is the output not inverted and is the amplification correct? Does the output voltage change for different loading resistances? Explain.

3. Build the inverting Op Amp circuit with $V_{CC} = 5$ V centered at 2.5 V, resistor $R_1 = 1$ k Ω (between the (-) terminal and the signal connection), resistor $R_2 = 3.3$ k Ω (between the (-) terminal and the output), and resistor $R_3 = 4.7$ k Ω (between the (+) terminal and the reference). Connect the function generator to the input with a square wave of 1 V peak-to-

peak and 1.0 kHz. Observe the output voltage with the oscilloscope, record the peak-to-peak output voltage, and plot or sketch the output voltage curve. Calculate the percent difference between the actual peak-to-peak output voltage and the theoretical voltage value. Replace the R_2 resistor with a 4.7 k Ω resistor. Again, observe the output voltage with the oscilloscope, record the peak-to-peak output voltage, and plot or sketch the output voltage curve. Calculate the percent difference between the actual peak-to-peak output voltage and the theoretical voltage value. Place a load resistor $R_L = 4.7$ k Ω between the output and the reference and observe the output voltage again.

Q3: Does the circuit operation match the theoretical expectations, i.e. is the output inverted and is the amplification correct? Does the output voltage change for different loading resistances? Explain.

Technical Memorandum:

- Memorandum discussion:
 - (1) Describe, based on your observations, the operation of the buffer Op Amp circuit. Does the operation match theoretical expectations? (Q1) How is the output voltage limited?
 - (2) Describe, based on your observations, the operation of the non-inverting Op Amp circuit. Does the operation match theoretical expectations? (Q2) Does the loading resistor effect the operation? Explain.
 - (3) Describe, based on your observations, the operation of the inverting Op Amp circuit. Does the operation match theoretical expectations? (Q3) Does the loading resistor effect the operation? Explain.
- Appendix 1: Record or sketch the output voltage curve for the buffer Op Amp circuit with 1 V peak-to-peak input. Record or sketch the output voltage curve for the buffer Op Amp circuit as the input produces a limited output. Calculate the input current from the voltage across the input resistor
- Appendix 2: Record or sketch the output voltage curve for the non-inverting Op Amp circuit without and with a load resistor. Calculate the percent difference between the actual peak-to-peak output voltage and the theoretical voltage value. Record or sketch the output voltage curve for the inverting Op Amp circuit for both resistor cases. Also, plot or sketch the curve with an added load resistor. Calculate the percent difference between the actual peak-to-peak output voltage and the theoretical voltage value for all three curves.