

- Write the procedure to read from memory location 2Ch, write A5h to address 2Ch, then read from address 2Ch.

Procedure

- With the power off, set up the MCM 6810 so that it is in “write mode,” as depicted in Figure 10-1. Have your instructor check your circuit before turning the power on.
- Set switches SW2 – SW5 to correspond to your truth table’s first line inputs.
- Set switches SW7 – SW10 to correspond to your truth table’s first line outputs.
- Pulse switch SW1 low, in order to write the first line of data into the RAM.
- Repeat steps 2 through 4 for each line of your truth table.
- Remove the switches from the data lines and connect the data lines to the LEDs.
- Remove \overline{CS}_1 from SW1 and connect \overline{CS}_1 to ground. Do not remove R/ \overline{W} from SW1. At this point your setup should look like Figure 10-2.
- Verify that both functions are correct for all inputs by reading from the memory.
- After the instructor verifies that circuit is operating correctly, turn the power off and then back on. Read and record the truth table data from the memory.

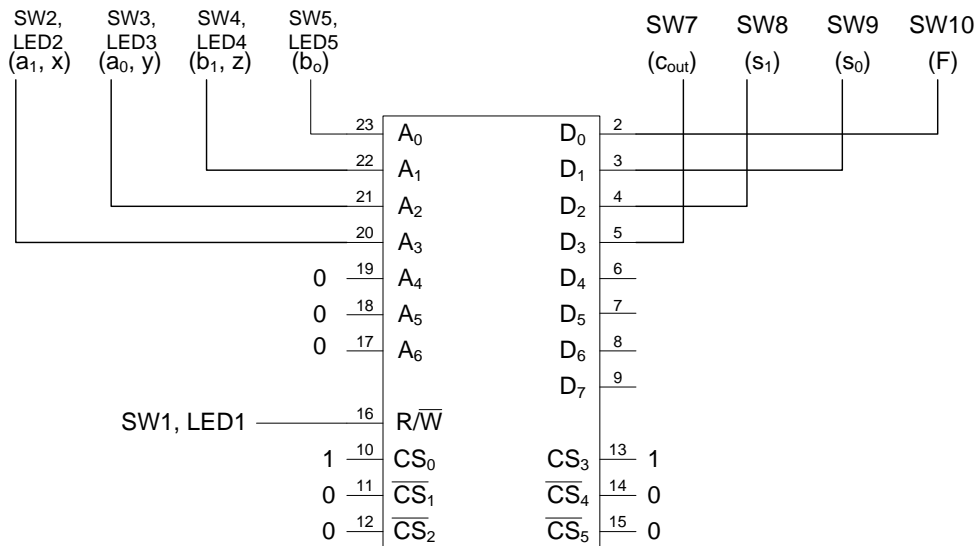


Figure 10-1: “Write Mode” Schematic Diagram

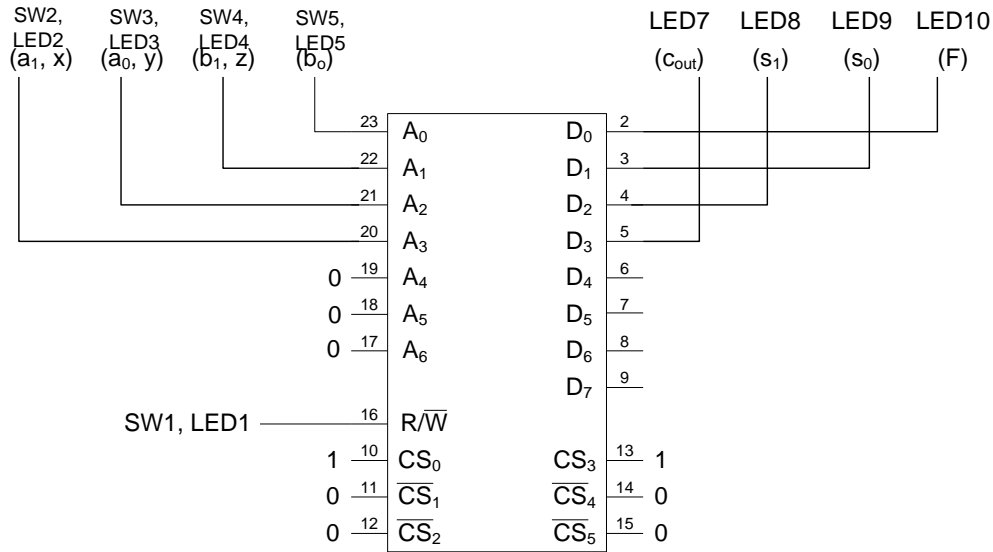


Figure 10-2: “Read Mode” Schematic Diagram

Questions

- 1) Discuss the advantages for using Ram for implementing combinational circuits.
- 2) Why are there so many chip select lines?
- 3) Would the MCM 6810 be a feasible alternative for any combinational logic circuits designed in previous laboratory experiments? Explain.
- 4) A memory circuit is going to be used to implement a combinational function in a commercial CD player. Which is more practical, RAM or ROM? Explain.