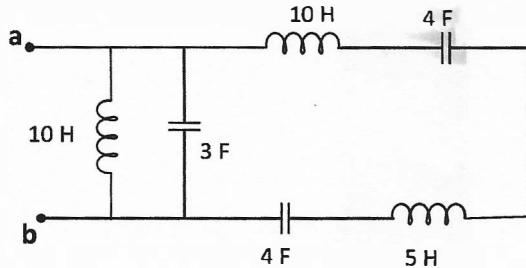



- (1) a) Determine the equivalent capacitance ( $C_{ab}$ ) and the equivalent inductance ( $L_{ab}$ ) seen from the terminals a - b. (9pts)



$$C_{ab} = 3F \parallel [4F - 4F] = 3 + 2 = \boxed{5F}$$

$$L_{ab} = 10H \parallel [10H - 5H] = \frac{10(15)}{25} = \boxed{6H}$$

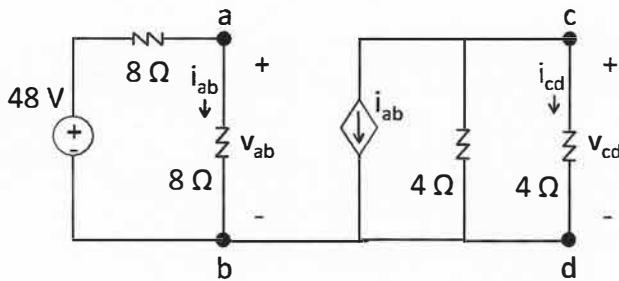- b) In the circuit below, calculate the unknown currents and voltages:  $i_{ab}$ ,  $v_{ab}$ ,  $i_{cd}$ , and  $v_{cd}$ . (16pts)



$$\text{Voltage divider: } v_{ab} = \frac{8}{8+8} \cdot 48 = \boxed{24V}$$

$$\text{Ohm's law: } i_{ab} = \frac{v_{ab}}{8} = \frac{24}{8} = \boxed{3A}$$

$$\text{Current divider: } i_{cd} = \frac{4}{4+4} (-i_{ab}) = \boxed{-1.5A}$$

$$\text{Ohm's law: } v_{cd} = 4 i_{cd} = 4(-1.5) = \boxed{-6V}$$

$$C_{ab} = \boxed{5F}$$

$$L_{ab} = \boxed{6H}$$

$$i_{ab} = \boxed{3A}$$


$$v_{ab} = \boxed{24V}$$

$$i_{cd} = \boxed{-1.5A}$$

$$v_{cd} = \boxed{-6V}$$

(2) For the circuit below,

a) Write a set of node voltage equations for the following circuit in matrix form. (13 pts)

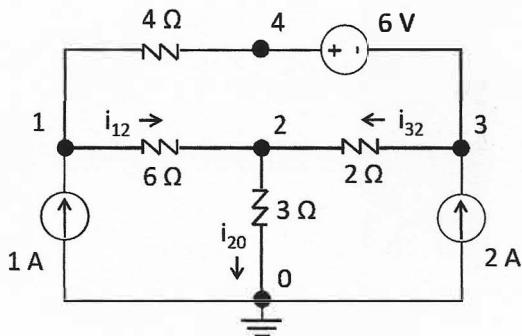b) Given that  $v_1 = 17 \text{ V}$  and  $v_2 = 9 \text{ V}$ , calculate  $i_{12}$ ,  $i_{20}$ , and  $i_{32}$ . (12 pts)

$$v_1, v_2, v_3, v_4$$

$$V_{src} : v_4 - v_3 = 6$$

$$[-v_3 + v_4 = 6] \rightarrow (1)$$

$$KCL @ 1 : \frac{v_1 - v_4}{4} + \frac{v_1 - v_2}{6} = 1 \times 12$$

$$[5v_1 - 2v_2 - 3v_4 = 12] \rightarrow (ii)$$

$$KCL @ 2 : \frac{v_2 - v_1}{6} + \frac{v_2}{3} + \frac{v_2 - v_3}{2} = 0 \times 6$$

$$[-v_1 + 6v_2 - 3v_3 = 0] \rightarrow (iii)$$

$$KCL @ 0 : 1 - \frac{v_2}{3} - 2 = 0 \Rightarrow [v_2 = 9] \rightarrow (iv)$$

OR  $KCL @ SN(3-4) : \frac{v_3 - v_2}{2} + \frac{v_4 - v_1}{4} = 2 \times 4$

$$[-v_1 - 2v_2 + 2v_3 + v_4 = 8] \rightarrow (v)$$

$$i_{12} = \frac{v_1 - v_2}{6} = \frac{17 - 9}{6} = \frac{4}{3} \text{ A}$$

$$\begin{bmatrix} 0 & 0 & -1 & 1 \\ 5 & -2 & 0 & -3 \\ -1 & 6 & -3 & 0 \\ 0 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 6 \\ 12 \\ 0 \\ 9 \end{bmatrix}$$

OR  $\begin{bmatrix} 0 & 0 & -1 & 1 \\ 5 & -2 & 0 & -3 \\ -1 & 6 & -3 & 0 \\ -1 & -2 & 2 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 6 \\ 12 \\ 0 \\ 8 \end{bmatrix}$

$$i_{20} = \frac{v_2}{3} = \frac{9}{3} = 3 \text{ A}$$

 $KCL @ 2 :$ 

$$i_{32} + i_{12} - i_{20} = 0$$

$$\therefore i_{32} = i_{20} - i_{12} = \frac{4}{3} \text{ A}$$


$$i_{12} = \underline{\underline{4/3 \text{ A}}} \quad i_{20} = \underline{\underline{3 \text{ A}}} \quad i_{32} = \underline{\underline{5/3 \text{ A}}}$$

(3) For the circuit below,

a) Write a set of mesh current equations for the following circuit in matrix form. (13 pts)

b) Given that  $i_2 = -1\text{ A}$  and  $i_3 = 4\text{ A}$ , calculate the following:i. Voltage  $v_{ab}$  (4pts)

ii. Power absorbed by 5 A current source [note: no credit with wrong power sign convention]. (4pts)

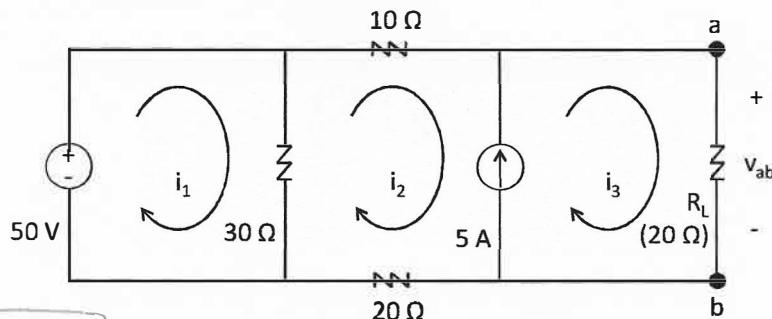iii. Power absorbed by the resistor  $R_L (= 20 \text{ ohm})$  [note: no credit with wrong power sign convention]. (4pts)

$$[-i_2 + i_3 = 5] \rightarrow (I)$$

$$\text{KVL @ } i_1 : -50 + 30i_1 - 30i_2 = 0 \Rightarrow [30i_1 - 30i_2 = 50] \rightarrow (II)$$

$$\text{KVL @ SM(2-3)} : 30i_2 - 30i_1 + 10i_2 + 20i_3 + 20i_2 = 0$$

$$\therefore [30i_1 + 60i_2 + 20i_3 = 0] \rightarrow (III)$$

$$V_{ab} = i_3 \cdot 20 = 20(4) = 80\text{V}$$

$$P_{5A} = -5 V_{ab} = -5(80) = -400\text{W} \quad P_{RL} = \frac{V_{ab}^2}{R_L} \text{ or } V_{ab} i_3 = 4(80) = 320\text{W}$$


$$\begin{bmatrix} 0 & -1 & 1 \\ 30 & -30 & 0 \\ -30 & 60 & 20 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 50 \\ 0 \end{bmatrix}$$

$$v_{ab} = 80\text{V} \quad \text{power (5A source)} = -400\text{W} \quad \text{power (R}_L\text{)} = 320\text{W}$$


(4) For the network below,

(a) Use a series of source transformations to determine and sketch the equivalent Thevenin circuit with respect to terminals  $a$  and  $b$  consisting of a voltage source and series resistance. (20 pts)

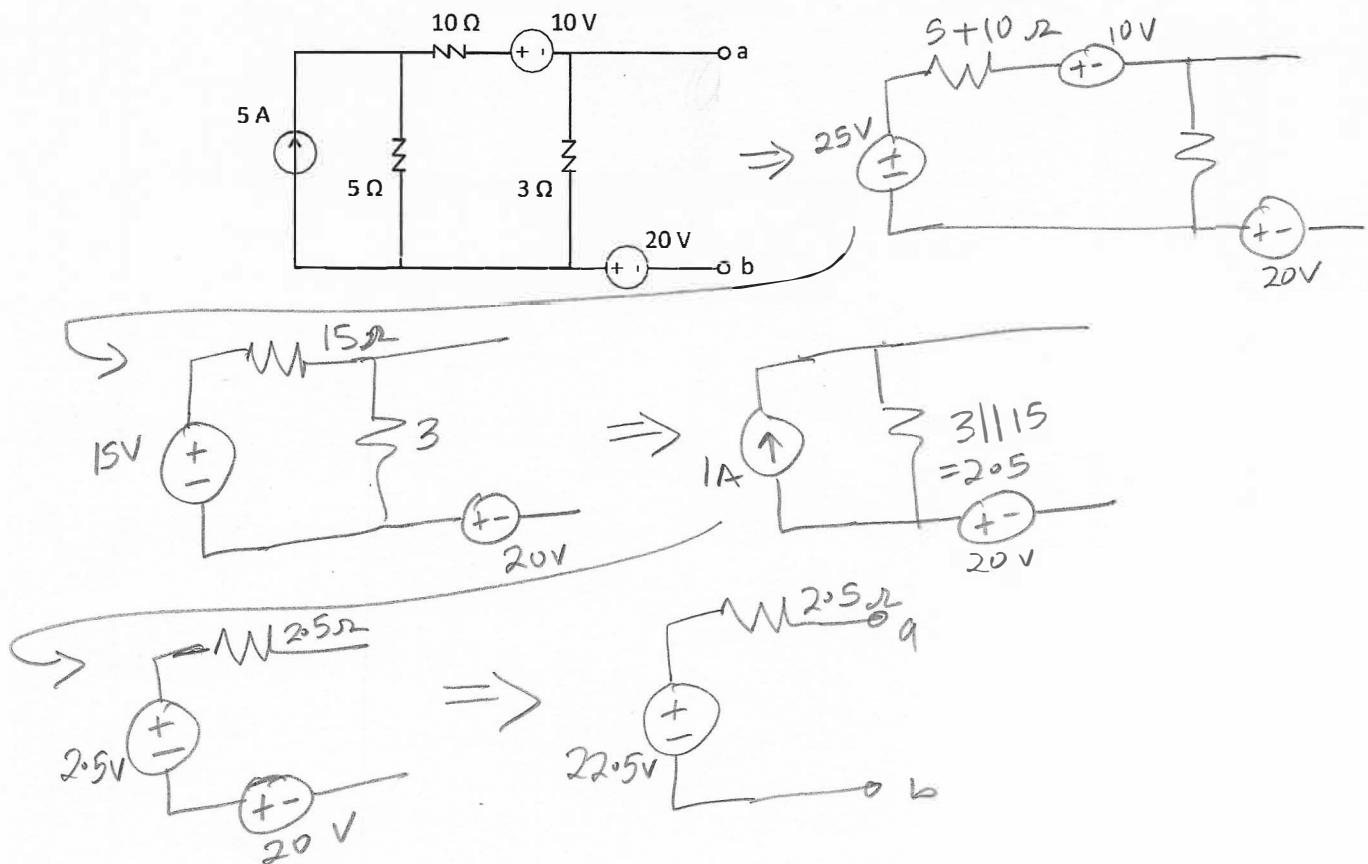(b) Sketch the equivalent Norton circuit based on your answer obtained in part (a). (5 pts)



Thevenin Equivalent Circuit

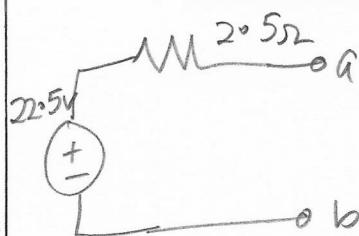

Norton Equivalent Circuit




(5) For the circuit below,

- a. Find and sketch the Thevenin equivalent circuit with respect to the terminals  $a$  and  $b$ . (15 pts)

- b. Find the load resistance,  $R_L$ , which should be attached between the end terminals  $a$  and  $b$  so that maximum power is delivered to the load. (3 pts)

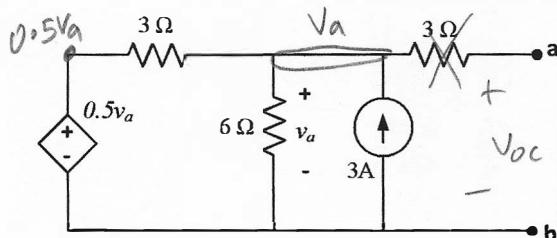- c. Calculate the value of the maximum power delivered to the load. (7pts)



$$R_L = R_{th} = 6\Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{9^2}{4(6)} = 3.375W$$


$$= 3.375W$$

$V_{th}$  directly  
 $V_{oc} = V_a$

$$KCL @ V_a: \frac{V_a - 0.5V_a}{3} + \frac{V_a}{6} - 3 = 0 \Rightarrow 2V_a = 18 \Rightarrow V_a = 9V$$

$$\therefore V_{oc} = 9V$$

$R_{th}$  directly:

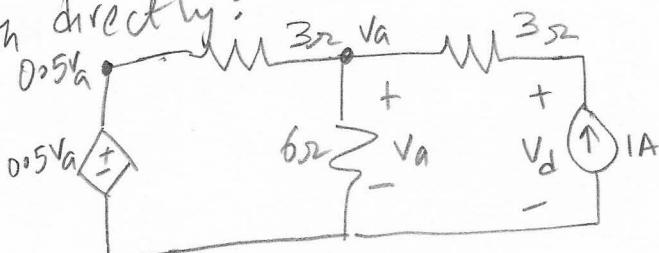

$$R_{th} = \frac{V_d}{I}$$

$$KVL: -V_a - 3 + V_d = 0$$


$$V_d = 3 + V_a \rightarrow (1)$$

$$KCL @ V_a: \frac{V_a}{6} + \frac{V_a - 0.5V_a}{3} = 1 \Rightarrow 2V_a = 6 \Rightarrow V_a = 3V$$

$$\therefore V_d = 6V$$

$$\therefore R_{th} = 6\Omega$$

Alternate:

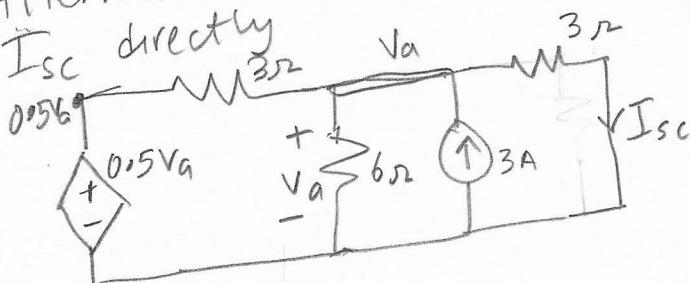

$$I_{sc} = \frac{V_a}{3}$$


KCL @ Va:

$$\frac{V_a}{6} + \frac{V_a}{3} + \frac{V_a - 0.5V_a}{3} = 3 \Rightarrow 4V_a = 18$$

$$\therefore V_a = 18/4$$

$$\therefore I_{sc} = \frac{18}{12}$$

$$= \frac{3}{2}A$$

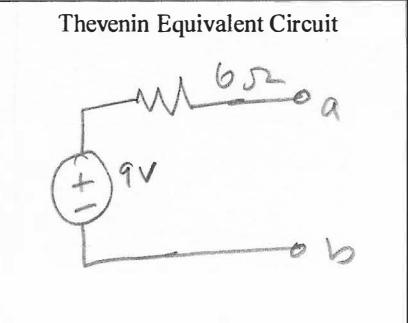

$$\therefore R_{th} = \frac{V_{oc}}{I_{sc}}$$


$$= 6\Omega$$

Same

$$R_L = \underline{\underline{6\Omega}}$$



$$P_{max} = \underline{\underline{3.375W}}$$

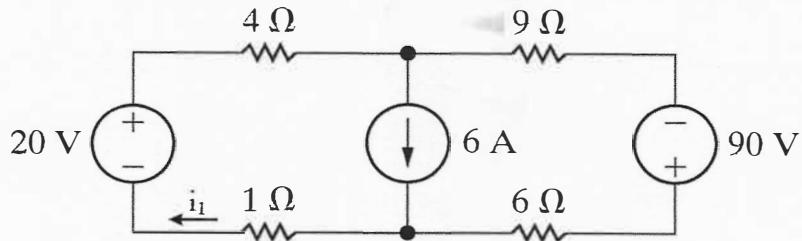(6) Use superposition to calculate the current,  $i_1$ , in the following circuit. Sketch the circuits for each step of the superposition. (25 pts.)



$$i_1 = i_{1/20V} + i_{1/6A} + i_{1/90V}$$



$i_{1/20V}$ :

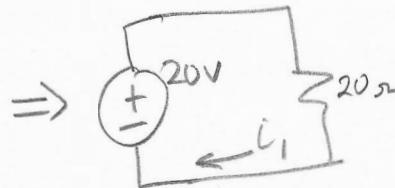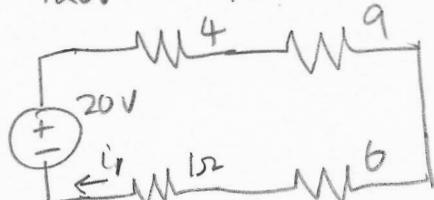

Ohm's law



$$i_1 = \frac{20}{20} = 1A$$

$i_{1/6A}$ :

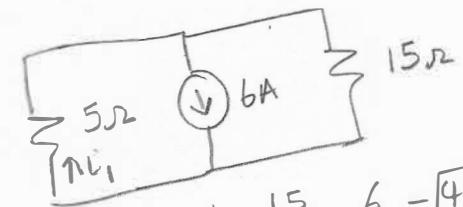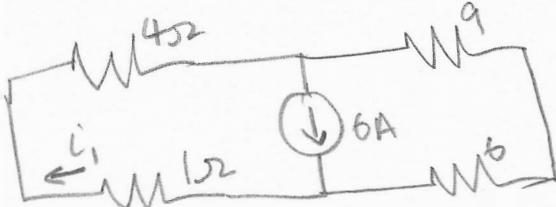

$$\text{current divider: } i_1 = \frac{15}{15+5} \cdot 6 = 4.5A$$

$i_{1/90V}$ :

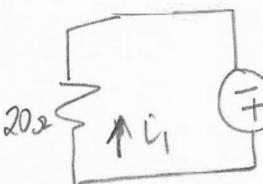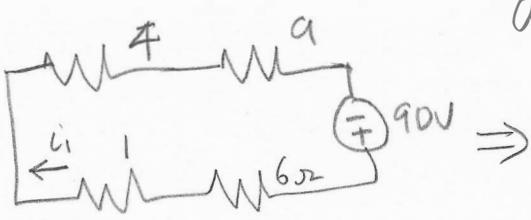

Ohm's law

$$i_1 = \frac{90}{20} = 4.5A$$

$$\therefore i_1 = 1 + 4.5 + 4.5$$


$$= 10A$$

$i_1 =$

10A

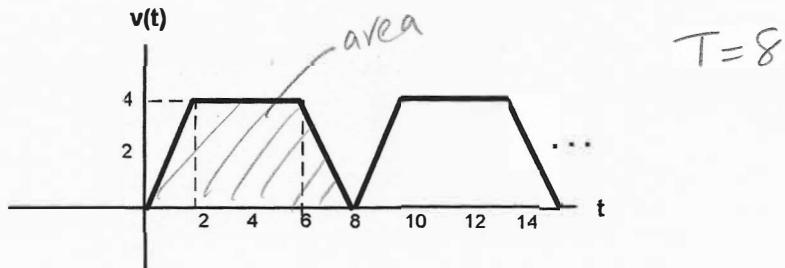(7) Given the following voltage signal;

- Write an expression for  $v(t)$  utilizing the step unit and ramp functions over the interval  $0 < t < T$  where  $T$  is the period.
- Calculate the average voltage  $V_{avg}$  over the period (10 pts.)
- Calculate the average power dissipation  $P_{av}$  when  $v(t)$  is applied across a resistor of 4 ohms. (8 pts.)



$$(a) v(t) = 2r(t) - 2r(t-2) + 2r(t-6)$$

$$(b) V_{avg} = \frac{1}{T} \int_T v(t) dt = \frac{1}{8} \left[ \int_0^2 2t dt + \int_2^6 4 dt + \int_6^8 (16-2t) dt \right]$$

$$= \frac{1}{8} (8+16) = \boxed{3V} \quad \text{area under graph} \quad \text{also valid}$$

$$(c) P_{av} = \frac{V_{rms}^2}{4}; \quad V_{rms} = \sqrt{\frac{1}{T} \int_T v^2 dt} = \sqrt{\frac{1}{8} \left( \int_0^2 4t^2 dt + \int_2^6 16 dt + \int_6^8 (16-2t)^2 dt \right)}$$


$$\therefore V_{rms}^2 = \frac{1}{8} \left( 10.67 + 64 + 10.67 \right) = 10.67$$

$$\therefore P_{av} = \frac{10.67}{4} = \boxed{2.67 W}$$

$$v(t) = \underline{\underline{2r(t) - 2r(t-2) + 2r(t-6)}}$$

$$V_{avg} = \underline{\underline{3V}} \quad P_{av} = \underline{\underline{2.67W}}$$

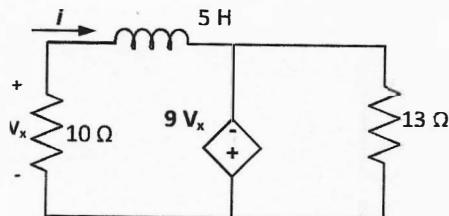- (8) For the source-free circuit below, given that  $i(0^+) = 80 \text{ A}$ , determine the following:
- The differential equation in terms of  $i(t)$ . (15 pts.)
  - The time constant  $\tau$  (3 pts.)
  - The current through the inductor  $i(t)$  for  $t > 0$ . (7 pts.)



KVL @ left loop

$$-V_x + 5 \frac{di}{dt} - 9V_x = 0$$

$$\frac{di}{dt} - 2V_x = 0 \quad \text{--- (1)}$$

From ohm's law

$$V_x = -10i$$


$$\therefore \boxed{\frac{di}{dt} + 20i = 0}$$

b)  $\tau = \frac{1}{20} \text{ s}$

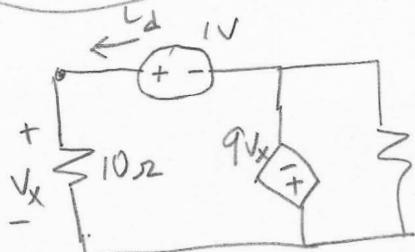c)  $i(t) = Ae^{-t/\tau} = Ae^{-20t} ; A = i(0^+) = 80$

$$\therefore \boxed{i(t) = 80e^{-t/2} \text{ A}}$$

Alternate  
simplify ckt:  
using  $R_{th}$



$$R_{th} = \frac{1}{i_d}$$

$$\text{KVL: } -V_x + 1 - 9V_x = 0$$

$$V_x = \frac{1}{10}$$

$$\text{Ohm's law: } \frac{V_x}{10} = i_d \Rightarrow i_d = \frac{1}{100}$$

$$\therefore R_{th} = \frac{1}{i_d} = \boxed{100 \Omega}$$

simplified  
ckt



$$\Rightarrow \tau = L/R = \frac{5}{100}$$

$$= \boxed{1/20 \text{ s}} \text{ same}$$


differential equation:  $\boxed{\frac{di}{dt} + 20i = 0}$

time constant  $\tau = \boxed{1/20 \text{ s}}$


$i(t) = \boxed{80e^{-t/2} \text{ A}}$

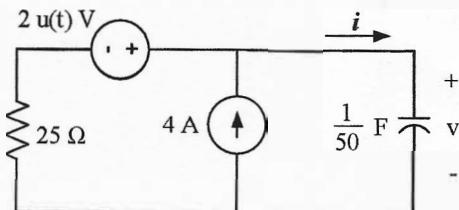(9) For the circuit below,

- Determine the initial condition  $v(0^+)$ . (5 pts.)
- Write the differential equation for the circuit in terms of  $v(t)$  for  $t > 0$ . (10 pts.)
- Determine the complete solution,  $v(t)$  for  $t > 0$ . (10 pts.)




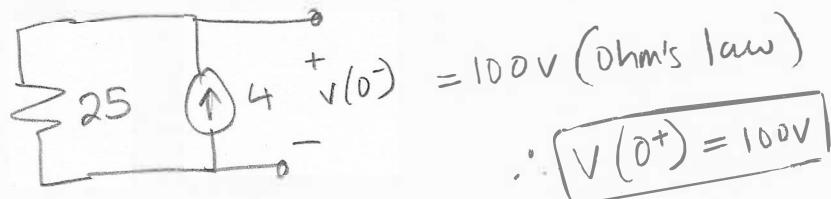a)  $v(0^+) = v(0^-)$  go to  $\text{at } t < 0 \text{ i.e. } t = 0^-$



$$\therefore \boxed{v(0^+) = 100V}$$

b)  $t > 0$  diff eqn?

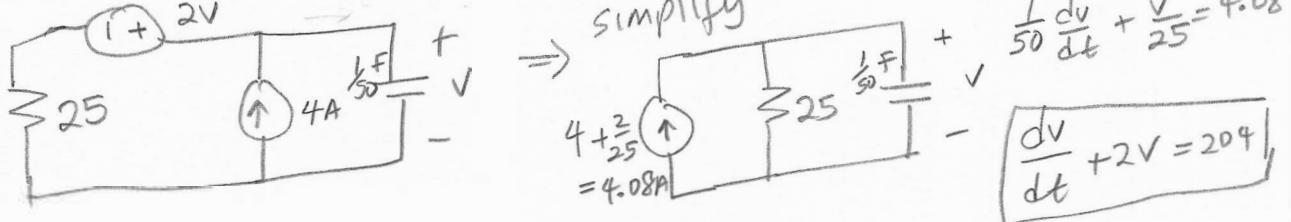

c)  $v(t)$ ?  $v(t) = v_n + v_p$

$$v_n = Ae^{-t/2} = Ae^{-2t}$$

$$v_p = K \quad \therefore v'_p = k \\ \text{plug into diff eqn}$$

$$2K = 204 \Rightarrow K = 102$$

$$\therefore \boxed{v_p = 102V}$$

$$\therefore v(t) = Ae^{-2t} + 102$$

use I.C to find A:  $v(0) = A + 102 = 100$

$$\therefore A = -2 \quad \therefore \boxed{v(t) = -2e^{-2t} + 102 V}$$


$$v(0^+) = \boxed{100V}$$

$$\text{differential equation: } \boxed{v' + 2v = 204}$$

$$v(t) = \boxed{-2e^{-2t} + 102 V}$$

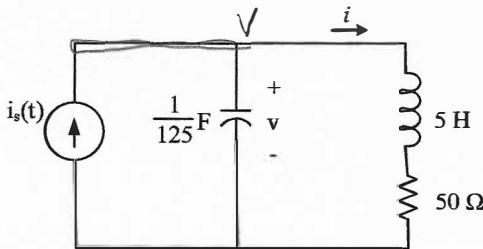(10) For the following RLC circuit, given that  $i_s = 12e^{-3t}$  A  $t > 0$ . Do the following:

- Write a differential equation, in terms of  $i$ , to find the current through the inductor  $t > 0$ . (3 pts)
- Find the form of the natural response  $i_n(t)$   $t > 0$ . (5 pts)
- Solve for the particular solution  $i_p(t)$   $t > 0$ . (5 pts)
- Solve for the general form of complete solution  $i(t)$   $t > 0$  in terms of the two undetermined coefficients only. (2 pts)



a) KCL @ V:

$$\frac{1}{125} \frac{dv}{dt} + i = i_s \quad (1)$$

KVL @ R Loop

$$-v + 5 \frac{di}{dt} + 50i = 0$$

$$\therefore v = 5 \frac{di}{dt} + 50i \quad (2)$$

 $\therefore$  plug (2) into (1)

$$\frac{1}{125} (5i'' + 50i') + i = i_s \times 25$$

$$i'' + 10i' + 25i = 25i_s$$

$$i'' + 10i' + 25i = 300e^{-3t}$$

b)  $i_n(t)$ ? characteristic eqn:  $s^2 + 10s + 25 = 0$   
 $s_{1,2} = -5$  repeated roots

$$\therefore i_n(t) = A_1 e^{-5t} + A_2 t e^{-5t}$$

c)  $i_p(t)$ ?  $i_p = Ke^{-3t} \Rightarrow i'_p = -3Ke^{-3t}; i''_p = 9Ke^{-3t}$ plug into diff eqn:  $9Ke^{-3t} + 10(-3K)e^{-3t} + 25Ke^{-3t} = 300e^{-3t}$   
 $\therefore 4K = 300 \Rightarrow K = 75 \therefore i_p = 75e^{-3t} \text{ A}$ d)  $i(t) = i_n(t) + i_p(t) = A_1 e^{-5t} + A_2 t e^{-5t} + 75e^{-3t} \text{ A}$ differential equation:  $i'' + 10i' + 25i = 300e^{-3t}$ 

$$i_n(t) = A_1 e^{-5t} + A_2 t e^{-5t} \text{ A} \quad i_p(t) = 75e^{-3t} \text{ A}$$

$$i(t) = A_1 e^{-5t} + A_2 t e^{-5t} + 75e^{-3t} \text{ A}$$