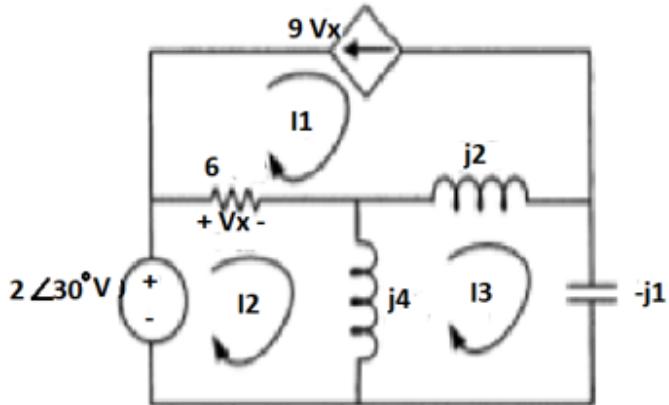


(1) a. Write a set of mesh current equations for the circuit to find  $I_1$ ,  $I_2$  and  $I_3$  in matrix form.

You must eliminate the control variable from your equations. (15)

b. Solve for phasor mesh current  $I_2$ . (5)

c. Express steady state mesh current  $i_2(t)$  in time domain if  $\omega=1250$  rad/s. (5)



$$\underline{\text{M1}}: \quad \tilde{I}_1 = -9 \tilde{V}_x ; \quad \tilde{V}_x = 6(\tilde{I}_2 - \tilde{I}_1)$$

$$\Rightarrow \tilde{I}_1 = -54(\tilde{I}_2 - \tilde{I}_1)$$

$$\Rightarrow 53\tilde{I}_1 - 54\tilde{I}_2 = 0 \quad -\textcircled{1}$$

$$\underline{\text{M2}}: \quad -2\angle 30^\circ + 6(\tilde{I}_2 - \tilde{I}_1) + j4(\tilde{I}_2 - \tilde{I}_3) = 0$$

$$-6\tilde{I}_1 + (6+j4)\tilde{I}_2 + (-j4)\tilde{I}_3 = 2\angle 30^\circ \quad -\textcircled{2}$$

$$\underline{\text{M3}}: \quad j4(\tilde{I}_3 - \tilde{I}_2) + j2(\tilde{I}_3 - \tilde{I}_1) - j1(\tilde{I}_3) = 0$$

$$(-j2)\tilde{I}_1 + (-j4)\tilde{I}_2 + (j5)\tilde{I}_3 = 0 \quad -\textcircled{3}$$

$$\begin{bmatrix} 53 & -54 & 0 \\ -6 & (6+j4) & -j4 \\ -j2 & -j4 & j5 \end{bmatrix} \begin{bmatrix} \tilde{I}_1 \\ \tilde{I}_2 \\ \tilde{I}_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 2\angle 30^\circ \\ 0 \end{bmatrix}$$

b)  $\tilde{I}_1 = 2.43 \angle 127.77^\circ A$

$\boxed{\tilde{I}_2 = 2.387 \angle 127.77^\circ A}$

$\tilde{I}_3 = 2.88 \angle 127.77^\circ A$

[c]  $i_2(t) = 2.39 \cos(1250t + 127.77^\circ) A$

Simultaneous equation solution if not using calculator

$$\textcircled{1} \Rightarrow \tilde{I}_1 = \frac{54}{53} \tilde{I}_2$$

$$\begin{aligned}\textcircled{3} \Rightarrow \tilde{I}_3 &= \frac{(j4)\tilde{I}_2 + (j2)\tilde{I}_1}{(j5)} \\ &= \frac{4}{5}\tilde{I}_2 + \frac{2}{5}\tilde{I}_1 \\ &= \frac{4}{5}\tilde{I}_2 + \frac{2}{5}\left(\frac{54}{53}\right)\tilde{I}_2\end{aligned}$$


$$\tilde{I}_3 = \frac{64}{53} \tilde{I}_2$$

$$\textcircled{2} \Rightarrow -6\left(\frac{54}{53}\right)\tilde{I}_2 + (6+j4)\tilde{I}_2 + (-j4)\frac{64}{53}\tilde{I}_2 = 2 \angle 30^\circ$$

$$(0.838 \angle -97.77^\circ)\tilde{I}_2 = (2 \angle 30^\circ)$$

$$\Rightarrow \tilde{I}_2 = \frac{2 \angle 30^\circ}{0.838 \angle -97.77^\circ} = \boxed{2.387 \angle 127.77^\circ A}$$

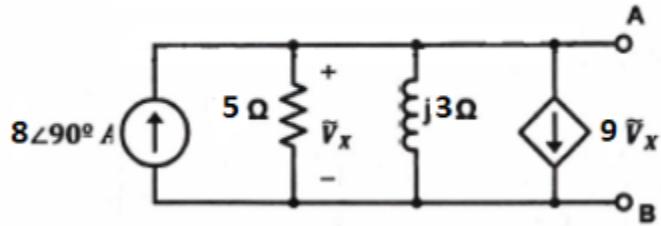- (2) Find and sketch the Thevenin Equivalent Circuit with respect to terminals A and B.  
 Calculate the Thevenin voltage and impedance. (25 points)



$$\tilde{V}_{AB} = \tilde{V}_x \quad \text{KCL at top node:}$$

$$-8\angle 90^\circ + \frac{\tilde{V}_{AB}}{5} + \frac{\tilde{V}_{AB}}{j3} + 9\tilde{V}_{AB} = 0$$

$$\tilde{V}_{AB} \left( \frac{1}{5} + \frac{1}{j3} + 9 \right) = 8\angle 90^\circ \Rightarrow \tilde{V}_{AB} = \frac{8\angle 90^\circ}{9.21\angle 2.07}$$


$$\boxed{\tilde{V}_{AB} = 0.869\angle 92.07^\circ \text{ V}}$$

$$Z_{Th}:$$


$$Z_{Th} = \frac{\tilde{V}_{AB}}{I_{AB}} = \frac{\tilde{V}_{AB}}{1\angle 0^\circ} \quad (\text{Ohm's Law})$$

$$\tilde{V}_{AB} = \frac{1\angle 0^\circ}{9.21\angle 2.07} = .109\angle 2.07^\circ$$

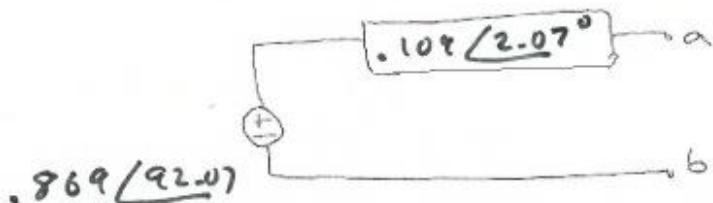
$$Z_{Th} = .109\angle 2.07^\circ \Omega \quad \text{or } 0.1089 + j0.0039 \Omega$$



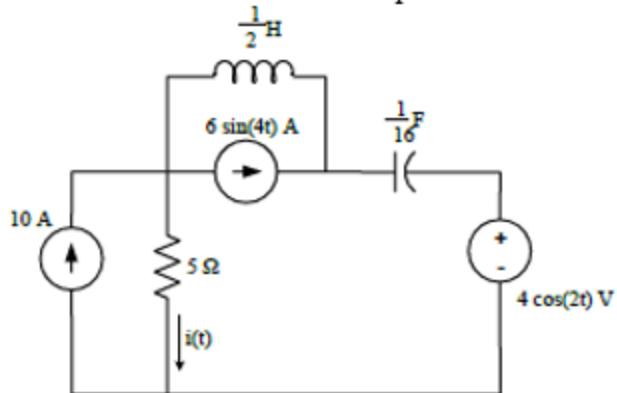- (3) For the following circuit, determine the time domain current,  $i(t)$  using Superposition.  
 Show/draw the circuit used for each part of the solution. (25)



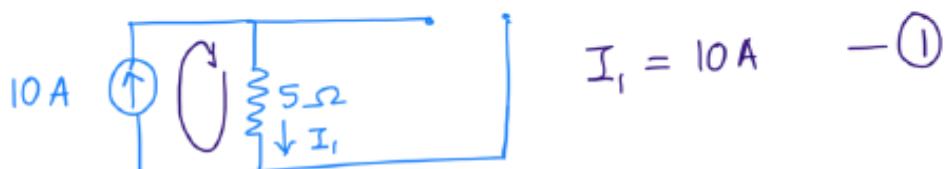
$$\cdot \text{DC} \Rightarrow \omega = 0 \quad Z_C \rightarrow \infty, \quad Z_L = 0$$



$$\cdot \omega = 4 \text{ rad/s} \quad Z_C = [j(4)(\frac{1}{16})]^{-1} = -j4 \Omega$$

$$Z_L = j(4)(\frac{1}{2}) = j^2 \Omega$$

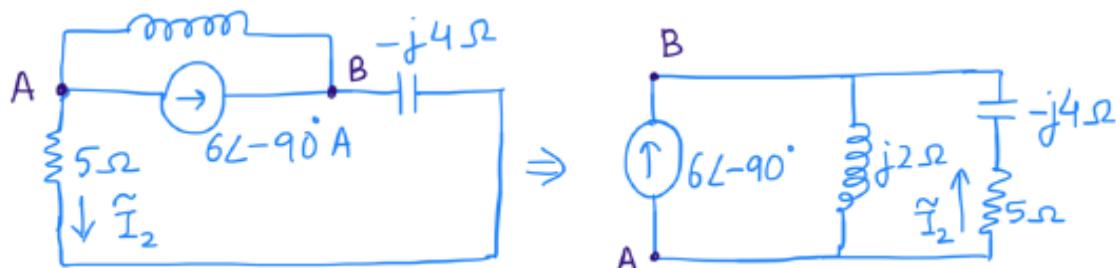


$$\tilde{I}_2 = -(6L-90^\circ) \left[ \frac{j^2 / (5-j4)}{(5-j4)} \right]$$

$$= (6L-90^\circ) \left( \frac{0.69 + j2.28}{5-j4} \right)$$

$$\tilde{I}_2 = 2.23 \angle -158.199^\circ A \quad \text{or} \quad -2.23 \angle 21.8^\circ A$$

$$i_2(t) = 2.23 \cos(4t - 158.199^\circ) A \quad -\textcircled{2}$$

•  $\omega = 2 \text{ rad/s}$

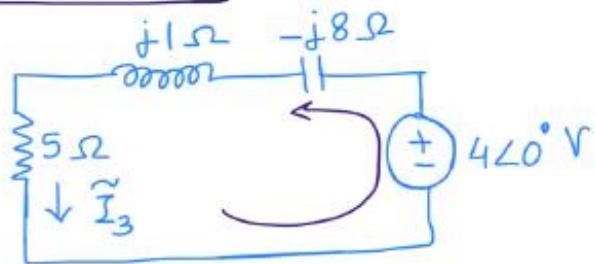

$$\begin{aligned}\tilde{I}_3 &= \tilde{I}_m \\ &= \frac{4 \angle 0^\circ}{5 - j7}\end{aligned}$$

$$\tilde{I}_3 = 0.465 \angle 54.46^\circ A$$

$$i_3(t) = 0.465 \cos(2t + 54.46^\circ) A \quad -\textcircled{3}$$

$$\textcircled{1}, \textcircled{2}, \textcircled{3} \Rightarrow i(t) = I_1 + i_2(t) + i_3(t)$$

$$i(t) = \underline{10 + 2.23 \cos(4t - 158.199^\circ) + 0.465 \cos(2t + 54.46^\circ)} A$$

Name: \_\_\_\_\_

- (4) A load draws  $|S| = 10,000 \text{ VA}$  from a 60-Hz sinusoidal source at a power factor of 0.707 leading. (5 points each below)

- (1) What is the average power delivered to the load?
- (2) What is the reactive power delivered to the load?
- (3) If  $V_{rms} = 120 \text{ volt}$ , what is the peak current,  $I_m$ ?
- (4) What is the complex power  $S$ ?
- (5) What is the load impedance  $Z$ ?

$$(1) P = \frac{|S| \cos \theta}{10,000} = \frac{10,000 \cdot 0.707}{10,000} = 7070 \text{ watt}$$

$$(2) Q = |S| \sin \theta = |S| \sqrt{1 - \cos^2 \theta} = \sqrt{10,000 \cdot (1 - 0.707^2)} = -7070 \text{ VAR}$$

$$(3) |S| = \left| \frac{1}{2} \tilde{V} \tilde{I}^* \right| = \frac{1}{2} V_m I_m \rightarrow I_m = 117.85 \text{ A}$$

$$(4) S = P + jQ = 7070 - j7070$$

$$(5) Z = \frac{\tilde{V} \tilde{I}^*}{\tilde{I}^2} = \frac{1}{2} I_m^2 Z$$

$$\begin{aligned} Z &= \frac{2 \tilde{S}}{I_m^2} = 2 \left[ \frac{7070(1-j)}{117.85^2} \right] = 2 [0.509(1-j)] \\ &= 1.018 (1-j) \end{aligned}$$

Problem #5: In the circuit below, an inductive load draw 1000 watt at "power factor",  $\text{PF}=0.9$  lagging from a  $120 \text{ V rms}$  source. In an effort to raise the power factor seen by the source, a small capacitive load is placed in parallel with the inductive load. The capacitive load draw 10 watt at  $\text{PF}=0.02$  leading,

(10pts) (1) Find the complex power supplied by the source,  $S_s$ .

(5pts) (2) Find the rms current supplied by the source,  $I_{\text{rms}}$ .

(5pts) (3) Find the rms current supplied to the inductive load,  $I_{1,\text{rms}}$ .

(5pts) (4) Find total impedance,  $Z$ , with respect to the source.


$$(a) \tilde{S}_s = \tilde{S}_1 + \tilde{S}_2$$

$$\tilde{S}_1 = P_1 + jQ_1$$

$$= \frac{1}{2} V_m I_m \cos(\omega t + \phi) + j \frac{1}{2} V_m I_m \sin(\omega t + \phi)$$

$$= 1000 + j \left( \frac{1000}{0.9} \right) \cdot 0.4358$$
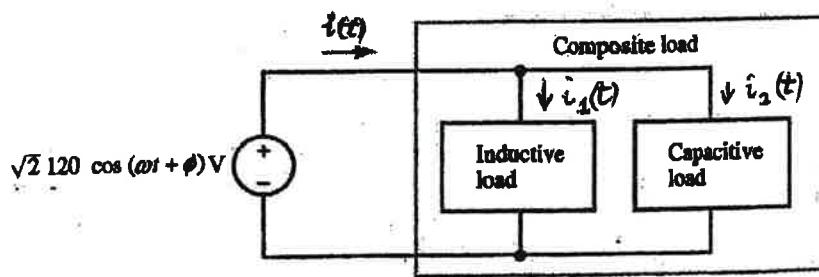
$$= 1000 + j 484.3 \quad (= 1111.1 \angle 25.84^\circ)$$



$$\tilde{S}_2 = 10 - j \left( \frac{10}{0.02} \right) \sqrt{1 - (0.02)^2} = 10 - j 499.9 \quad (= 500 \angle -88.85^\circ)$$

$$\tilde{S}_{\text{tot}} = \tilde{S}_1 + \tilde{S}_2 = 1010 - j 15.6 \quad \text{VA} \quad (= 1010.1 \angle -0.88^\circ)$$

$$(b) |\tilde{S}_s| = \frac{1}{2} V_m I_m \sqrt{V_m^2 + I_m^2} \rightarrow I_{\text{rms}} = \frac{|S_s|}{V_{\text{rms}}} = \frac{|1010 - j 15.6|}{120} \quad (= 8.42 \text{ A rms})$$

$$(c) |\tilde{S}_1| = \frac{1}{2} V_m I_m = (\underline{120}) \cdot I_{\text{rms}}, \quad I_{1,\text{rms}} = \frac{1111.1}{120} = 9.26 \text{ A rms}$$

$$\underline{1111.1} = V_{\text{rms}} I_{\text{rms}}$$

$$\tilde{S}_s = \frac{1}{2} \tilde{V} \tilde{I}^* = \frac{1}{2} \frac{\tilde{V} \tilde{I}}{\tilde{I}^*} = \frac{1}{2} \frac{\tilde{S}}{\tilde{Z}} \quad \tilde{Z} = \frac{2 \tilde{S}}{|\tilde{I}|^2} = \frac{2 (1010 - j 15.6)}{(8.42)^2} = \frac{1010 - j 15.6}{(8.42)^2}$$

$$I_m^2 = (\underline{9.26})^2 \quad (= 14.25 - j 0.22)$$

$$(d) \quad \tilde{I}^2$$

$$(\underline{14.25} - j 0.22)$$

# #6 Alternative

EE 2120 Final Exam



Dec. 17, 2020

Name: \_\_\_\_\_

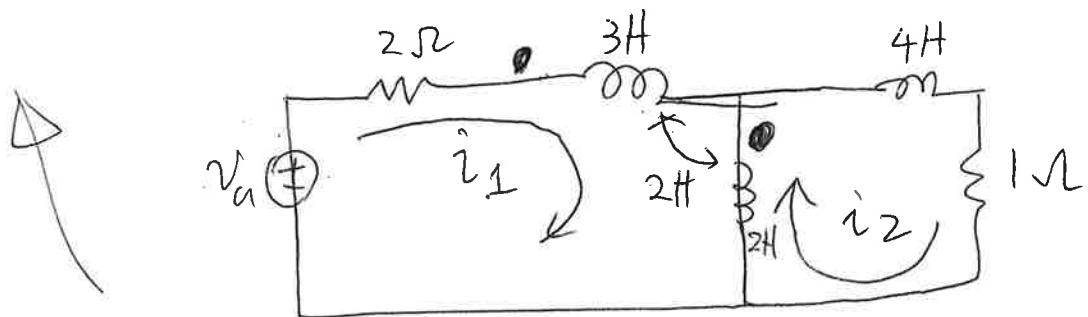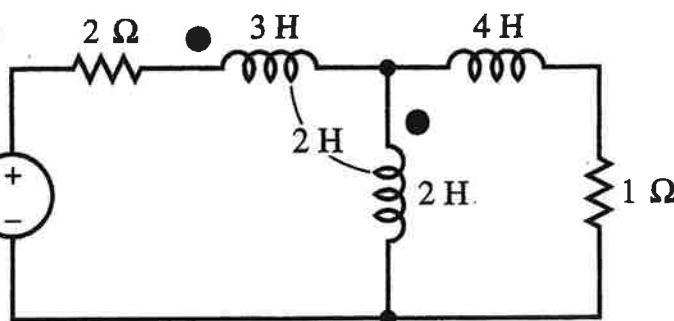- (6) Write two mesh current equations for the following circuit with mutual inductance  $M=2H$  as indicated in the following figure.

Ans:

$$\begin{vmatrix} 9\frac{d}{dt} + 2 & -4\frac{d}{dt} \\ -4\frac{d}{dt} & 1 + 6\frac{d}{dt} \end{vmatrix} \begin{vmatrix} i_1 \\ i_2 \end{vmatrix} = \begin{vmatrix} v_a \\ 0 \end{vmatrix}$$



KVL mesh 1

$$-v_a + i_2 + 3 \frac{di_1}{dt} + 2 \frac{d}{dt}(i_1 - i_2)$$

$$+ 2 \underbrace{\frac{d}{dt}(i_1 - i_2)}_{\text{mutual inductance from } 2H} + 2 \underbrace{\frac{di_1}{dt}}_{\text{Mutual inductance for } 3H} = 0$$

KVL mesh 2

$$4 \frac{di_2}{dt} + i_2 + 2 \frac{d}{dt}(i_2 - i_1) + 2 \underbrace{\frac{d(-i_1)}{dt}}_{\text{mutual inductance}} = 0$$

the same sign

(7) The transfer function in s domain,  $H(s)$  of a circuit is given by

$$H(s) = \frac{I_o}{V_s} = \frac{(s+2)^2}{(s+3)(s^2 + 2s + 10)}$$

- a. If the input  $v_s(t) = 5e^{-3t} \cos(2t + 30^\circ)$  V, find the output  $i_o(t)$ . (15 points)  
 b. Identify the location of poles and zeros and sketch the pole-zero plot for the transfer function. (10 points)

$$V_s = 5 \angle 30^\circ \text{ V}$$

$$s = -3 + j2$$

(a)  $I_o = H(s) V(s)$

$$= \frac{(-3+j2+2)^2}{(-3+j2+3)((-3+j2)^2 + 2(-3+j2) + 10)} \times 5 \angle 30^\circ$$

$$= 1.038 \angle -145.24^\circ \text{ A}$$

$$i_o(t) = 1.038 e^{-3t} \cos(2t - 145.24^\circ) \text{ A}$$

(b) Location of Zeros:  $s_{z_1} = -2$  (twice).

Location of Poles:  $s_{p_1} = -3$


$$s_{p_2} = -1+j3 \text{ and } s_{p_3} = -1-j3$$

$$i_o(t) = 1.038 e^{-3t} \cos(2t - 145.24^\circ) \text{ A}$$

Location of poles: -2 (twice)

Location of zeros: -3, -1+j3 and -1-j3

Pole-zero plot:

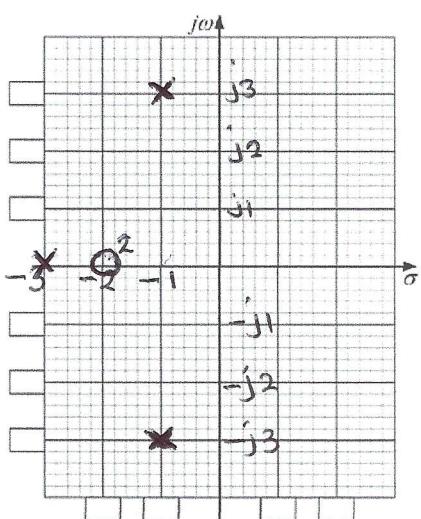

K = 1

Problem Score

/ 25

(8) The transfer function in frequency domain of a circuit,  $H(j\omega)$  is given by

$$H(j\omega) = \frac{V_{out}}{I_{in}} = \frac{(1 + j3\omega)}{(18 - 48\omega^2 + j20\omega)}$$

- (a) a. Develop the second order differential equation which models the circuit. (10 points)  
 b. If the input  $i_{in}(t) = 50\sin(10t + 90^\circ)$ A, find the output  $v_{out}(t)$ . (15 points)

$$H(j\omega) = \frac{V_{out}}{I_{in}} = \frac{(1 + j3\omega)}{(18 - 48\omega^2 + j20\omega)}$$

$$18 + 48(j\omega)^2 + 20j\omega V_{out} = (1 + 3(j\omega)) I_{in}$$

$$j\omega \rightarrow D \Rightarrow \frac{d}{dt}$$

$$(48 \frac{d^2}{dt^2} + 20 \frac{d}{dt} + 18) V_{out} = (1 + 3 \frac{d}{dt}) i_{in}$$

(b)  $i_{in}(t) = 50\sin(10t + 90^\circ)$  Amperes  $= 50\cos 10t$  A

$$I_{in} = 50\angle 0^\circ$$
 A  $\omega = 10$  rad/s

$$V_{out} = H(j\omega) \cdot I_{in}$$

$$= \frac{(1 + j3(10))}{(18 - 48(10)^2 + j(20)(10))} \times 50\angle 0^\circ$$

$$V_{out} = 0.314 \angle -89.51^\circ$$


$$v_{out} = 0.314 \cos(10t - 89.51^\circ) V$$

$$= 0.314 \sin(10t - 0.5^\circ) V$$

Differential Equation =  $(48 \frac{d^2}{dt^2} + 20 \frac{d}{dt} + 18) V_{out} = (1 + 3 \frac{d}{dt}) i_{in}$

$$v_{out}(t) = 0.314 \cos(10t - 89.51^\circ) V \text{ or } 0.314 \sin(10t - 0.5^\circ) V$$

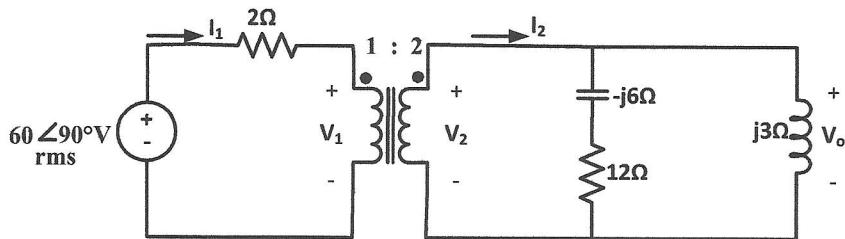(9) For the ideal transformer circuit below,



- Find the currents  $I_1$  and  $I_2$ . (10 Points)
  - Find the voltage  $V_1$ ,  $V_2$  and  $V_o$ . (10 Points)
  - The complex power supplied by the source  $\tilde{S}$ . (5 Points)
- (Note: Your answers should be in the polar form)

(a)

$$Z_L = j3 \parallel (12 - j6) = \frac{(j3)(12 - j6)}{(12 - j3)} = 3.25 \angle 77.47^\circ \Omega (0.706 + j3.177 \Omega)$$

$$Z_{in} = 2 + \frac{0.706 + j3.177}{2^2} = 2.176 + j0.794 \Omega = 2.317 \angle 20.04^\circ \Omega$$

$$I_1 = \frac{V_s}{Z_{in}} = \frac{60 \angle 90^\circ}{2.317 \angle 20.04} = 25.9 \angle 69.96^\circ A$$

$$I_2 = \frac{I_1}{2} = 12.95 \angle 69.96^\circ A$$

(b)

$$60 \angle 90^\circ = 2I_1 + V_1$$

$$V_1 = (60 \angle 90^\circ) - 2(25.9 \angle 69.96^\circ)$$

$$= 21.06 \angle 147.44^\circ V$$

$$V_2 = 2V_1 = 42.12 \angle 147.44^\circ V$$

$$V_o = V_2 = 42.12 \angle 147.44^\circ V$$

$$\tilde{S} = V_s I_1^* = (60 \angle 90^\circ)(25.9 \angle -69.96)$$

$$= 1554 \angle 20.04 \text{ VA}$$

$$I_1 = 25.9 \angle 69.96^\circ A$$

$$V_2 = 42.12 \angle 147.44^\circ V$$

$$I_2 = 12.95 \angle 69.96^\circ A$$

$$V_o = 42.12 \angle 147.44^\circ V$$

$$V_1 = 21.06 \angle 147.44^\circ V$$

$$\tilde{S} = 1554 \angle 20.04 \text{ VA}$$

KEY


(10) A balanced three-phase system consists of a source with a line-to-line voltage of 210V connected to the parallel combination of a delta-load  $Z_{\Delta} = 24 - j30\Omega$  and a wye-load  $Z_Y = 12 + j5\Omega$  through a line impedance  $Z_{line} = 1 + j1\Omega$ .

- a. Draw the per-phase equivalent circuit representation. Take phase A line-to-neutral voltage to be your angle reference. (7 points)

Converting the delta load into a wye load;  $Z_{Y_2} = \frac{Z_{\Delta}}{3} = \frac{24 - j30}{3} = 8 - j10\Omega$

$$V_{an} = \frac{210 \angle 0^\circ}{\sqrt{3}}$$

$$= 121.24 \angle 0^\circ V$$

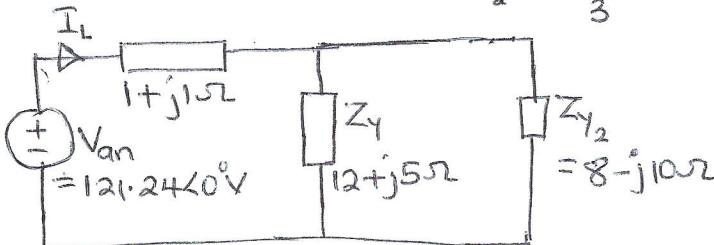

- b. Determine the magnitude of the line current of the combined loads. (8 points)

$$Z_p = Z_Y || Z_{Y_2} = \frac{(12 + j5)(8 - j10)}{20 - j5} = 8.076 \angle -14.68^\circ \Omega \quad (7.812 - j2.047 \Omega)$$

$$Z_T = Z_p + Z_{line} = 8.812 - j1.047 = 8.874 \angle -6.78^\circ \Omega$$

$$I_L = \frac{V_{an}}{Z_T} = \frac{210}{(\sqrt{3} \times 8.874 \angle -6.78^\circ)} = 13.66 \angle 6.78^\circ A$$

$$|I_L| = 13.66 A$$

- c. Determine the magnitude of the current flowing through the delta-connected load. (5 points)

$$I_{\Delta} = \frac{12 + j5}{(12 + j5) + (8 - j10)} \times 13.66 \angle 6.78^\circ \quad (\text{By current division})$$

$$= 8.614 \angle 43.44^\circ A$$

$$|I_{\Delta}| = 8.614 A$$

- d. Determine the magnitude of the current flowing through the wye-connected load. (5 points)

$$I_Y = \frac{8 - j10}{(12 + j5) + (8 - j10)} \times 13.66 \angle 6.78^\circ \quad (\text{By current division})$$

$$= 8.486 \angle -30.52^\circ A$$

$$|I_Y| = 8.486 A$$

$$|I_L| = 13.66 A \quad |I_{\Delta}| = 8.614 A \quad |I_Y| = 8.486 A$$