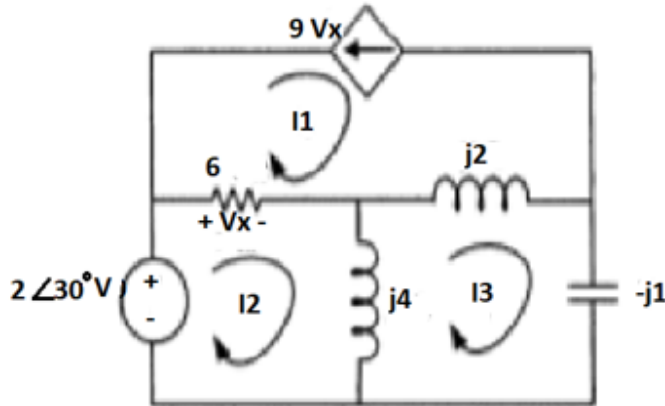


- (1) a. Write a set of mesh current equations for the circuit to find I_1 , I_2 and I_3 in matrix form. You must eliminate the control variable from your equations. (15)
 b. Solve for phasor mesh current I_2 . (5)
 c. Express steady state mesh current $i_2(t)$ in time domain if $\omega=1250$ rad/s. (5)



a. M1: $\tilde{I}_1 = -9\tilde{V}_x$; $\tilde{V}_x = 6(\tilde{I}_2 - \tilde{I}_1)$

$\Rightarrow \tilde{I}_1 = -54(\tilde{I}_2 - \tilde{I}_1)$

$\Rightarrow 53\tilde{I}_1 - 54\tilde{I}_2 = 0 \quad \text{--- (1)}$

M2: $-2\angle 30^\circ + 6(\tilde{I}_2 - \tilde{I}_1) + j4(\tilde{I}_2 - \tilde{I}_3) = 0$

$-6\tilde{I}_1 + (6+j4)\tilde{I}_2 + (-j4)\tilde{I}_3 = 2\angle 30^\circ \quad \text{--- (2)}$

M3: $j4(\tilde{I}_3 - \tilde{I}_2) + j2(\tilde{I}_3 - \tilde{I}_1) - j1(\tilde{I}_3) = 0$

$(-j2)\tilde{I}_1 + (-j4)\tilde{I}_2 + (j5)\tilde{I}_3 = 0 \quad \text{--- (3)}$

$$\begin{bmatrix} 53 & -54 & 0 \\ -6 & (6+j4) & -j4 \\ -j2 & -j4 & j5 \end{bmatrix} \begin{bmatrix} \tilde{I}_1 \\ \tilde{I}_2 \\ \tilde{I}_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 2\angle 30^\circ \\ 0 \end{bmatrix}$$

$$b) \quad \tilde{I}_1 = 2.43 \angle 127.77^\circ \text{ A}$$

$$c) i_2(t) = 2.39 \cos(1250t + 127.77^\circ) \text{ A}$$

$$\tilde{I}_2 = 2.387 \angle 127.77^\circ \text{ A}$$

$$\tilde{I}_3 = 2.88 \angle 127.77^\circ \text{ A}$$

Simultaneous equation solution if not using calculator

$$\textcircled{1} \Rightarrow \tilde{I}_1 = \frac{54}{53} \tilde{I}_2$$


$$\begin{aligned} \textcircled{3} \Rightarrow \tilde{I}_3 &= \frac{(j4) \tilde{I}_2 + (j2) \tilde{I}_1}{(j5)} \\ &= \frac{4}{5} \tilde{I}_2 + \frac{2}{5} \tilde{I}_1 \\ &= \frac{4}{5} \tilde{I}_2 + \frac{2}{5} \left(\frac{54}{53} \right) \tilde{I}_2 \end{aligned}$$

$$\tilde{I}_3 = \frac{64}{53} \tilde{I}_2$$

$$\begin{aligned} \textcircled{2} \Rightarrow -6 \left(\frac{54}{53} \right) \tilde{I}_2 + (6+j4) \tilde{I}_2 + (-j4) \frac{64}{53} \tilde{I}_2 &= 2 \angle 30^\circ \\ (0.838 \angle -97.77^\circ) \tilde{I}_2 &= (2 \angle 30^\circ) \end{aligned}$$

$$\Rightarrow \tilde{I}_2 = \frac{2 \angle 30^\circ}{0.838 \angle -97.77^\circ} = \underline{2.387 \angle 127.77^\circ \text{ A}}$$

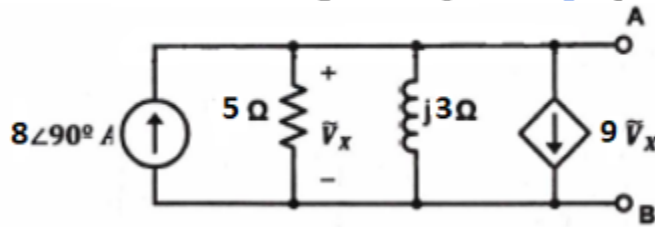- (2) Find and sketch the Thevenin Equivalent Circuit with respect to terminals A and B. Calculate the Thevenin voltage and impedance. (25 points)



$\tilde{V}_{AB} = \tilde{V}_x$ KCL at top node:

$$-8\angle 90^\circ + \frac{\tilde{V}_{AB}}{5} + \frac{\tilde{V}_{AB}}{j3} + 9\tilde{V}_{AB} = 0$$

$$\tilde{V}_{AB} \left(\frac{1}{5} + \frac{1}{j3} + 9 \right) = 8\angle 90^\circ \Rightarrow \tilde{V}_{AB} = \frac{8\angle 90^\circ}{9.21\angle 2.07^\circ}$$

$$\tilde{V}_{AB} = 0.869\angle 92.07^\circ \text{ V}$$


Z_{Th} :

$Z_{Th} = Z_{AB} = \frac{\tilde{V}_{AB}}{1\angle 0^\circ}$ (Ohm's Law)


KCL $\frac{\tilde{V}_{AB}}{5} + \frac{\tilde{V}_{AB}}{j3} + 9\tilde{V}_{AB} = 1\angle 0^\circ$

$$\tilde{V}_{AB} = \frac{1\angle 0^\circ}{9.21\angle 2.07^\circ} = 0.109\angle 2.07^\circ$$
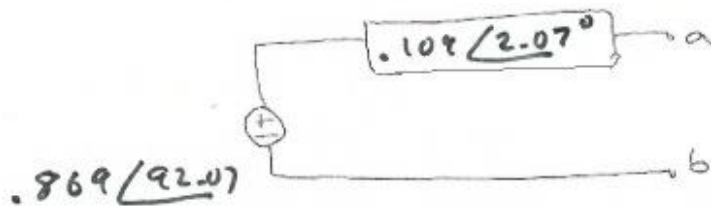
$$Z_{Th} = \frac{0.109\angle 2.07^\circ}{1\angle 0^\circ} \Omega \quad \text{or } 0.1089 + j0.0039 \Omega$$



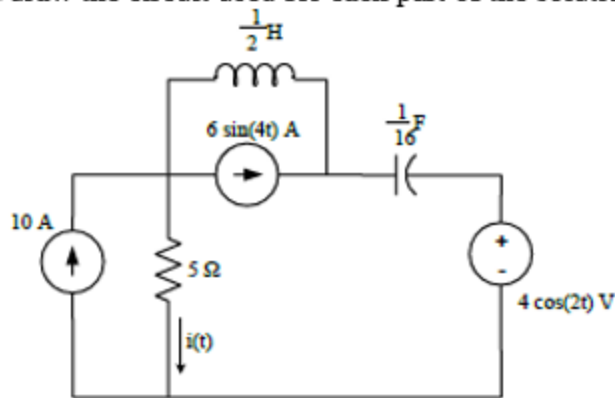
- (3) For the following circuit, determine the time domain current, $i(t)$ using Superposition. Show/draw the circuit used for each part of the solution. (25)



• DC $\Rightarrow \omega = 0$ $Z_C \rightarrow \infty$, $Z_L = 0$



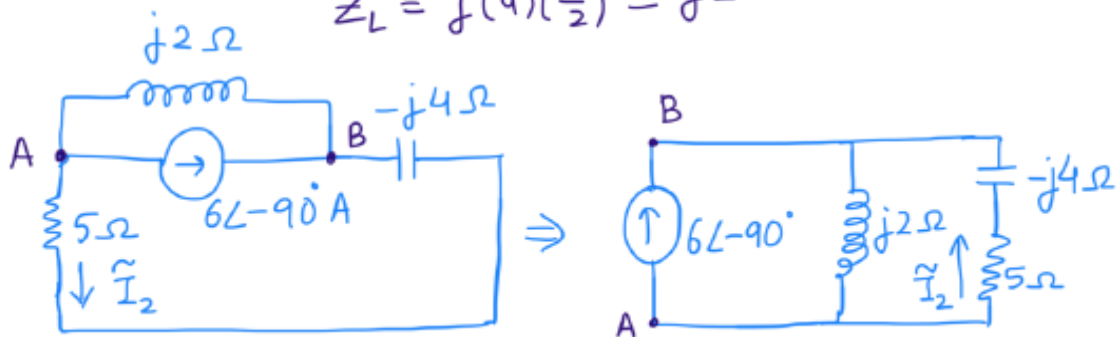• $\omega = 4 \text{ rad/s}$ $Z_C = [j(4)(\frac{1}{16})]^{-1} = -j4 \Omega$
 $Z_L = j(4)(\frac{1}{2}) = j2 \Omega$




$$\tilde{I}_2 = -(6\angle -90^\circ) \left[\frac{j2 \parallel (5-j4)}{5-j4} \right]$$

$$= (6\angle 90^\circ) \left(\frac{0.69 + j2.28}{5-j4} \right)$$

$$\tilde{I}_2 = 2.23 \angle -158.199^\circ \text{ A} \quad \text{or} \quad -2.23 \angle 21.8^\circ \text{ A}$$

$$i_2(t) = 2.23 \cos(4t - 158.199^\circ) \text{ A} \quad \text{--- (2)}$$

• $\omega = 2 \text{ rad/s}$

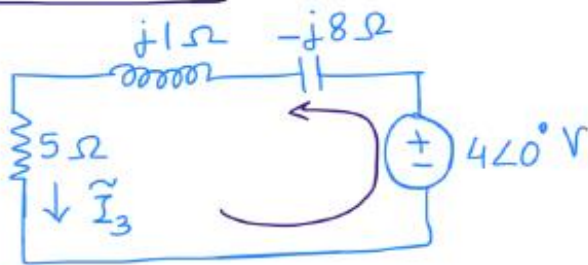

$$\begin{aligned} \tilde{I}_3 &= \tilde{I}_m \\ &= \frac{4 \angle 0^\circ}{5 - j7} \end{aligned}$$

$$\tilde{I}_3 = 0.465 \angle 54.46^\circ \text{ A}$$

$$i_3(t) = 0.465 \cos(2t + 54.46^\circ) \text{ A} \quad \text{--- (3)}$$

$$\textcircled{1}, \textcircled{2}, \textcircled{3} \Rightarrow i(t) = I_1 + i_2(t) + i_3(t)$$

$$i(t) = \underline{10 + 2.23 \cos(4t - 158.199^\circ) + 0.465 \cos(2t + 54.46^\circ) \text{ A}}$$

Name: _____

(4) A load draws $|S| = 10,000$ VA from a 60-Hz sinusoidal source at a power factor of 0.707 leading. (5 points each below)

- (1) What is the average power delivered to the load?
- (2) What is the reactive power delivered to the load?
- (3) If $V_{rms} = 120$ volt, what is the peak current, I_m ?
- (4) What is the complex power S ?
- (5) What is the load impedance Z ?

$$(1) \quad P = |S| \cos \theta = 7070 \text{ watt}$$

$\begin{array}{ccc} \parallel & \parallel & \\ 10,000 & 0.707 & \end{array}$

$$(2) \quad Q = |S| \sin \theta = -|S| \sqrt{1 - \cos^2 \theta} = -7070 \text{ VAR}$$

$\underline{\underline{\bar{S} = P + jQ}}$

$$(3) \quad |S| = \left| \frac{1}{2} \bar{V} \tilde{I}^* \right| = \frac{1}{2} \underbrace{V_m}_{120\sqrt{2}} I_m \rightarrow I_m = 117.85 \text{ A}$$

$\begin{array}{ccc} \parallel & \parallel & \\ 10,000 & & \end{array}$

$$(4) \quad \bar{S} = P + jQ = \underline{\underline{7070 - j7070}}$$

$$(5) \quad \bar{S} = \frac{1}{2} \underbrace{\tilde{V}}_{\tilde{I} \tilde{Z}} \tilde{I}^* = \frac{1}{2} I_m^2 \tilde{Z}$$

$$\tilde{Z} = \frac{1}{2} \frac{\bar{S}}{I_m^2} = \frac{1}{2} \left[\frac{7070(1-j)}{117.85^2} \right] = \frac{1}{2} [0.509(1-j)]$$

$$= 0.254(1-j)$$

Problem #5: In the circuit below, an inductive load draw 1000 watt at "power factor", PF=0.9 lagging from a 120 V rms source. In an effort to raise the power factor seen by the source, a small capacitive load is placed in parallel with the inductive load. The capacitive load draw 10 watt at PF=0.02 leading,

(10pts) (1) Find the complex power supplied by the source, \tilde{S}_s .

(5pts) (2) Find the rms current supplied by the source, I_{rms} .

(5pts) (3) Find the rms current supplied to the inductive load, $I_{1,rms}$.

(5pts) (4) Find total impedance, Z , with respect to the source.

$$(a) \tilde{S}_s = \tilde{S}_1 + \tilde{S}_2$$

$$\tilde{S}_1 = P_1 + jQ_1$$

$$= \frac{1}{2} V_m I_m \cos \theta + j \frac{1}{2} V_m I_m \sin \theta$$

$\frac{1000}{\cos \theta} = \frac{1000}{0.9}$
 $\sin \theta = \sqrt{1 - \cos^2 \theta} = \sqrt{1 - 0.9^2} = \sqrt{0.19} = 0.4358$

$$= 1000 + j \left(\frac{1000}{0.9} \right) \cdot 0.4358 = 1000 + j 484.3 \quad (= 1111.1 \angle 25.84^\circ)$$

$$\tilde{S}_2 = 10 - j \left(\frac{10}{0.02} \right) \sqrt{1 - (0.02)^2} = 10 - j 499.9 \quad (= 500 \angle -88.85^\circ)$$

$$\tilde{S}_{tot} = \tilde{S}_1 + \tilde{S}_2 = 1010 - j 15.6 \quad \text{VA} \quad (= 1010.1 \angle -0.88^\circ)$$


(b) $|\tilde{S}_s| = \frac{1}{2} V_m I_m \rightarrow I_{rms} = \frac{|S_s|}{V_{rms}} = \frac{|1010 - j 15.6|}{120} = 8.42 \text{ A rms}$

(c) $|\tilde{S}_1| = \frac{1}{2} V_m I_m = (120) \cdot I_{1,rms} \rightarrow I_{1,rms} = \frac{1111.1}{120} = 9.26 \text{ A (rms)}$

$$\tilde{S}_s = \frac{1}{2} \tilde{V} \tilde{I}^* = \frac{1}{2} Z \tilde{I} \tilde{I}^* = \frac{1}{2} |I|^2 Z \rightarrow Z = \frac{2 \tilde{S}_s}{|I|^2} = \frac{2(1010 - j 15.6)}{(\sqrt{2} \cdot 8.42)^2} = \frac{1010 - j 15.6}{(8.42)^2}$$

(d) $Z = \frac{1010 - j 15.6}{(8.42)^2} = 14.25 - j 0.22$

$$= 14.25 \angle -0.88^\circ$$

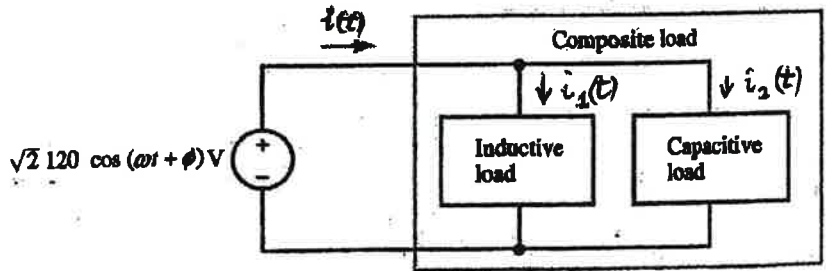

#6 Alternative

EE 2120 Final Exam



Dec. 17, 2020

Name: _____

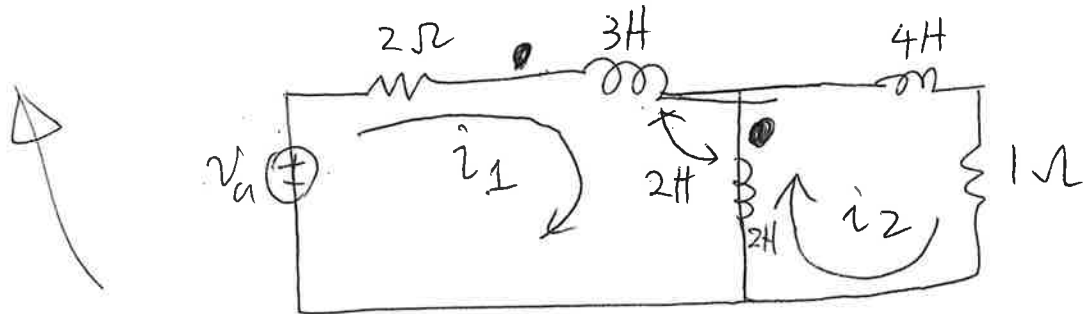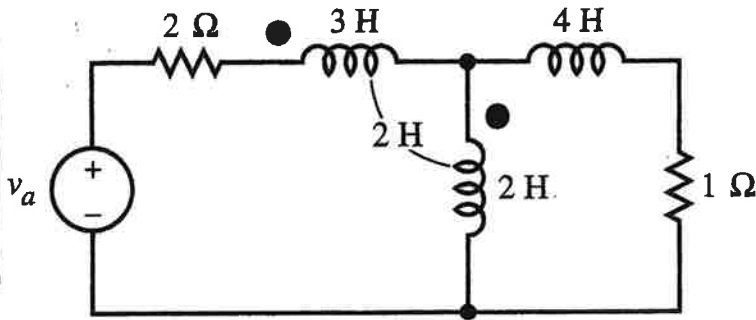(6) Write two mesh current equations for the following circuit with mutual inductance $M=2H$ as indicated in the following figure.

Ans:

$$\begin{vmatrix} 9\frac{d}{dt} + 2 & -4\frac{d}{dt} \\ -4\frac{d}{dt} & 1 + 6\frac{d}{dt} \end{vmatrix} \begin{vmatrix} i_1 \\ i_2 \end{vmatrix} = \begin{vmatrix} v_a \\ 0 \end{vmatrix}$$



KVL mesh 1

$$-v_a + i_1 2 + 3 \frac{di_1}{dt} + 2 \frac{d(i_1 - i_2)}{dt} = 0$$

$$+ 2 \frac{d(i_1 - i_2)}{dt} + 2 \frac{di_1}{dt} = 0$$

mutual inductance from 2H
Mutal inductance for 3H

KVL mesh 2

$$4 \frac{di_2}{dt} + i_2 + 2 \frac{d(i_2 - i_1)}{dt} + 2 \frac{d(-i_1)}{dt} = 0$$

the same sign
mutal inductan

(7) The transfer function in s domain, $H(s)$ of a circuit is given by

$$H(s) = \frac{I_o}{V_s} = \frac{(s+2)^2}{(s+3)(s^2+2s+10)}$$

$$V_s(s) = 5 \angle 30^\circ \text{ V}$$

$$s = -3 + j2$$

- If the input $v_s(t) = 5e^{-3t} \cos(2t + 30^\circ) \text{ V}$, find the output $i_o(t)$. (15 points)
- Identify the location of poles and zeros and sketch the pole-zero plot for the transfer function. (10 points)

$$\begin{aligned} \text{(a) } I_o &= H(s) V(s) \\ &= \frac{(-3+j2+2)^2}{(-3+j2+3)((-3+j2)^2+2(-3+j2)+10)} \times 5 \angle 30^\circ \\ &= 1.038 \angle -145.24^\circ \text{ A} \end{aligned}$$

$$i_o(t) = 1.038 e^{-3t} \cos(2t - 145.24^\circ) \text{ A}$$

(b) Location of zero: $s_{z_1} = -2$ (twice).


Location of poles: $s_{p_1} = -3$

$s_{p_2} = -1 + j3$ and $s_{p_3} = -1 - j3$.

$$i_o(t) = 1.038 e^{-3t} \cos(2t - 145.24^\circ) \text{ A}$$

Location of poles: -2 (twice)

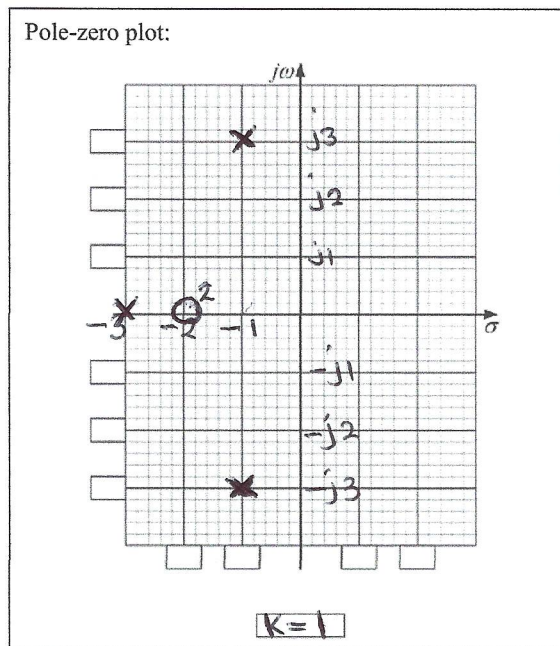Location of zeros: $-3, -1+j3$ and $-1-j3$



(8) The transfer function in frequency domain of a circuit, $H(j\omega)$ is given by

$$H(j\omega) = \frac{V_{out}}{I_{in}} = \frac{(1 + j3\omega)}{(18 - 48\omega^2 + j20\omega)}$$

(9)

- a. Develop the second order differential equation which models the circuit. (10 points)
 b. If the input $i_{in}(t) = 50\sin(10t + 90^\circ)$ A, find the output $v_{out}(t)$. (15 points)

$$\bar{H}(j\omega) = \frac{V_{out}}{I_{in}} = \frac{(1 + j3\omega)}{(18 - 48\omega^2 + j20\omega)}$$

$$18 + 48(j\omega)^2 + 20(j\omega)V_{out} = (1 + 3(j\omega))I_{in}$$

$$j\omega \rightarrow D \rightarrow \frac{d}{dt}$$

$$\left(48 \frac{d^2}{dt^2} + 20 \frac{d}{dt} + 18\right)V_{out} = \left(1 + 3 \frac{d}{dt}\right)i_{in}$$

(b) $i_{in}(t) = 50\sin(10t + 90^\circ)$ Amperes = $50\cos 10t$ A.

$I_{in} = 50\angle 0^\circ$ A $\omega = 10$ rad/s.

$$V_{out} = H(j\omega) \cdot \bar{I}_{in}$$

$$= \frac{(1 + j3(10))}{(18 - 48(10)^2 + j(20)(10))} \times 50\angle 0^\circ$$

$$V_{out} = 0.314 \angle -89.51^\circ \text{ V}$$


$$V_{out} = 0.314 \cos(10t - 89.51^\circ) \text{ V}$$

$$= 0.314 \sin(10t - 0.5^\circ) \text{ V}$$

Differential Equation = $\left(48 \frac{d^2}{dt^2} + 20 \frac{d}{dt} + 18\right)v_{out} = \left(1 + 3 \frac{d}{dt}\right)i_{in}$

$v_{out}(t) = 0.314 \cos(10t - 89.51^\circ) \text{ V}$ or $0.314 \sin(10t - 0.5^\circ) \text{ V}$

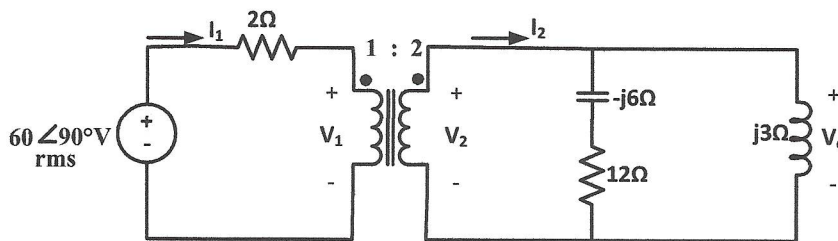(9) For the ideal transformer circuit below,



- Find the currents I_1 and I_2 . (10 Points)
 - Find the voltage V_1 , V_2 and V_0 . (10 Points)
 - The complex power supplied by the source \tilde{S} . (5 Points)
- (Note: Your answers should be in the polar form)

(a)

$$Z_L = j3 \parallel (12 - j6) = \frac{(j3)(12 - j6)}{(12 - j3)} = 3.25 \angle 77.47^\circ \Omega \quad (0.706 + j3.177)$$

$$Z_{in} = 2 + \frac{0.706 + j3.177}{2} = 2.176 + j0.794 \Omega = 2.317 \angle 20.04^\circ \Omega$$

$$I_1 = \frac{V_s}{Z_{in}} = \frac{60 \angle 90^\circ}{2.317 \angle 20.04^\circ} = 25.9 \angle 69.96^\circ \text{ A}$$

$$I_2 = \frac{I_1}{2} = 12.95 \angle 69.96^\circ \text{ A}$$

(b)

$$60 \angle 90^\circ = 2I_1 + V_1$$

$$V_1 = (60 \angle 90^\circ) - 2(25.9 \angle 69.96^\circ) = 21.06 \angle 147.44^\circ \text{ V}$$

$$V_2 = 2V_1 = 42.12 \angle 147.44^\circ \text{ V}$$

$$V_0 = V_2 = 42.12 \angle 147.44^\circ \text{ V}$$

$$(c) \tilde{S} = V_s I_1^* = (60 \angle 90^\circ)(25.9 \angle -69.96^\circ) = 1554 \angle 20.04^\circ \text{ VA}$$

$$I_1 = \underline{25.9 \angle 69.96^\circ \text{ A}}$$

$$V_2 = \underline{42.12 \angle 147.44^\circ \text{ V}}$$

$$I_2 = \underline{12.95 \angle 69.96^\circ \text{ A}}$$

$$V_0 = \underline{42.12 \angle 147.44^\circ \text{ V}}$$

$$V_1 = \underline{21.06 \angle 147.44^\circ \text{ V}}$$

$$\tilde{S} = \underline{1554 \angle 20.04^\circ \text{ VA}}$$


(10) A balanced three-phase system consists of a source with a line-to-line voltage of 210V connected to the parallel combination of a delta-load $Z_{\Delta} = 24 - j30\Omega$ and a wye-load $Z_Y = 12 + j5\Omega$ through a line impedance $Z_{line} = 1 + j1\Omega$.

- a. Draw the per-phase equivalent circuit representation. Take phase A line-to-neutral voltage to be your angle reference. (7 points)

Converting the delta load into a wye load; $Z_{Y_2} = \frac{Z_{\Delta}}{3} = \frac{24 - j30}{3} = 8 - j10\Omega$

$$V_{an} = \frac{210 \angle 0^\circ}{\sqrt{3}}$$

$$= 121.24 \angle 0^\circ \text{ V}$$

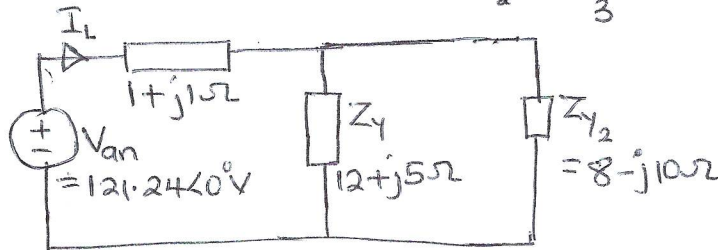

- b. Determine the magnitude of the line current of the combined loads. (8 points)

$$Z_p = Z_Y \parallel Z_{Y_2} = \frac{(12 + j5)(8 - j10)}{20 - j5} = 8.076 \angle -14.68^\circ \Omega \quad (7.812 - j2.047 \Omega)$$

$$Z_T = Z_p + Z_{line} = 8.812 - j1.047 = 8.874 \angle -6.78^\circ \Omega$$

$$I_L = \frac{V_{an}}{Z_T} = \frac{210}{\sqrt{3} \times 8.874 \angle -6.78^\circ} = 13.66 \angle 6.78^\circ \text{ A}$$

$$|I_L| = 13.66 \text{ A}$$

- c. Determine the magnitude of the current flowing through the delta-connected load. (5 points)

$$I_{\Delta} = \frac{12 + j5}{(12 + j5) + (8 - j10)} \times 13.66 \angle 6.78^\circ \quad (\text{By current division})$$

$$= 8.614 \angle 43.44^\circ \text{ A}$$

$$|I_{\Delta}| = 8.614 \text{ A}$$

- d. Determine the magnitude of the current flowing through the wye-connected load. (5 points)

$$I_Y = \frac{8 - j10}{(12 + j5) + (8 - j10)} \times 13.66 \angle 6.78^\circ \quad (\text{By current division})$$

$$= 8.486 \angle -30.52^\circ \text{ A}$$

$$|I_Y| = 8.486 \text{ A}$$

$$|I_L| = \underline{13.66 \text{ A}} \quad |I_{\Delta}| = \underline{8.614 \text{ A}} \quad |I_Y| = \underline{8.486 \text{ A}}$$