

Name: \_\_\_\_\_

Instructor: \_\_\_\_\_

Section/College: \_\_\_\_\_

Major:  Electrical Engineering  Computer Engineering (Check one)

## Electrical Engineering Advancement Exam II

SPRING SEMESTER 2021

CLOSED BOOK, CLOSED NOTES

2 HOUR TIME LIMIT

**CALCULATORS ARE ALLOWED**

(calculators without communication capability only)

**ELECTRONIC DEVICES WITH COMMUNICATION CAPABILITY**

**MAY NOT BE USED DURING THE EXAMINATION**

(electronic devices such as cell phone, pagers, and iPads)

**(If such devices ring or are visible,**


**a 10% penalty will be given for the first occurrence and exam failure for the second.)**

There are 10 problems: please look over the exam to make sure that you have 10 different problems. **Do any eight (8) problems!** Draw a large X through the two problems that you do not want to be graded. If you do not indicate which problems you want to leave out, the first 8 problems will be graded.

Do all work for each problem only on the page supplied for that problem (you may use both sides). **DO NOT**, for instance, continue Problem #3 on the back of Problem #2. Extra blank paper will be supplied if needed. If extra paper is used, show the additional work for each problem on a separate sheet, write your name and problem number on the sheet, and staple the extra sheet(s) to the appropriate problems.

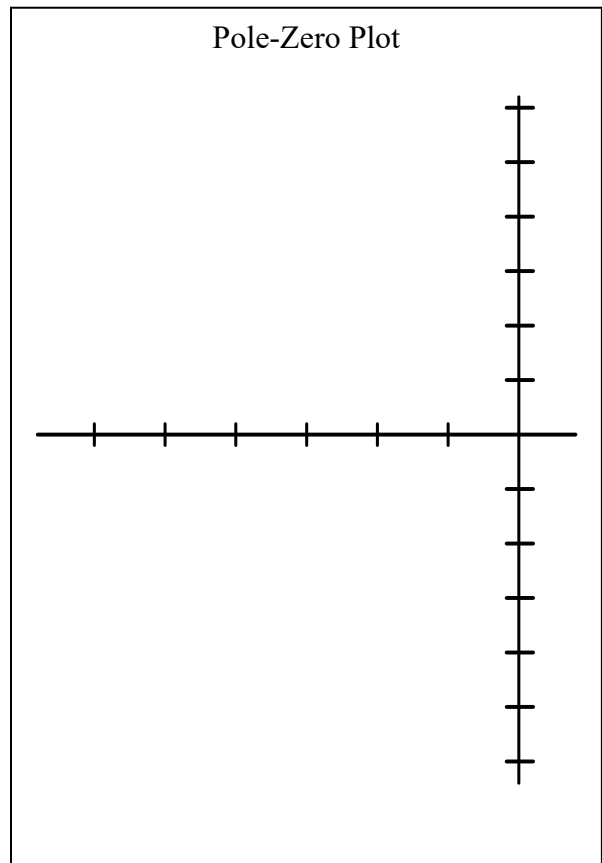(1) The transfer function for a particular circuit is  $H(s) = \frac{V_{out}}{I_{in}} = \frac{10s^2}{(s+3)(s+2+j)(s+2-j)}$ .

- What are the units of the transfer function? (1 pt.)
- Sketch and label the pole-zero plot. (8 pts.)
- Find the particular solution,  $v_{out}(t)$ , given the following input:  
 $i_{in}(t) = 10e^{-t} \cos(5t + 45^\circ) \text{ A}$ . (10 pts.)
- Determine the differential equation with relates the input and output. (6 pts.)




Transfer function units = \_\_\_\_\_

$v_{out}(t) =$  \_\_\_\_\_

differential equation: \_\_\_\_\_

(2) In the following filter,

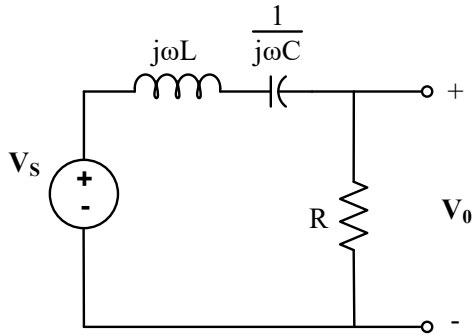

- Determine the magnitude of the transfer function,  $|H(j\omega)|$  in terms of  $R$ ,  $L$ ,  $C$  and  $\omega$ . (10 pts.)
- Determine  $|H(j0)|$  and  $|H(j\infty)|$ , the asymptotic behavior of the amplitude response. (4 pts.)
- Given that  $R=5\ \Omega$ , calculate the values of  $L$  and  $C$  necessary if the bandwidth is to be 2000 rad/sec and the center frequency is to be 40,000 rad/sec. (10 pts.)
- What type of filter is this: low-pass, high-pass, band-pass or band-reject? (1 pt.)

$$|H(j\omega)| = \underline{\hspace{10cm}}$$

$$|H(j0)| = \underline{\hspace{10cm}}$$


$$|H(j\infty)| = \underline{\hspace{10cm}}$$

$$L = \underline{\hspace{10cm}}$$

$$C = \underline{\hspace{10cm}}$$

Filter type (circle one):    low-pass    high-pass    band-pass    band-reject

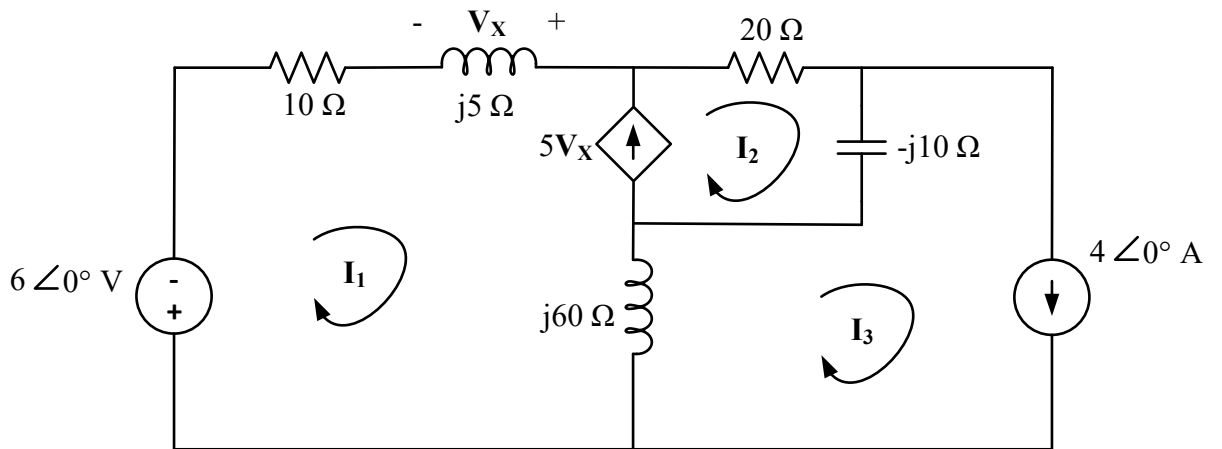
- (3) Write a set of phasor mesh current equations for the circuit to find  $\mathbf{I}_1$ ,  $\mathbf{I}_2$ , and  $\mathbf{I}_3$  in matrix form. You must eliminate the control variables from your equations. Do not solve.



[


$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} \phantom{0} \\ \phantom{0} \\ \phantom{0} \end{bmatrix}$$

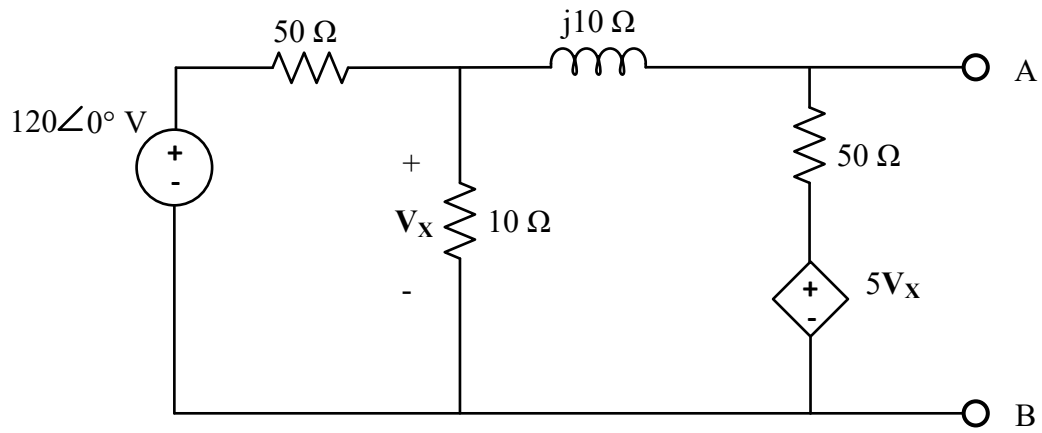(4) Calculate the open circuit voltage,  $V_{th}$  or  $V_{AB}$ , for the given circuit.



$V_{th}=V_{AB} =$  \_\_\_\_\_

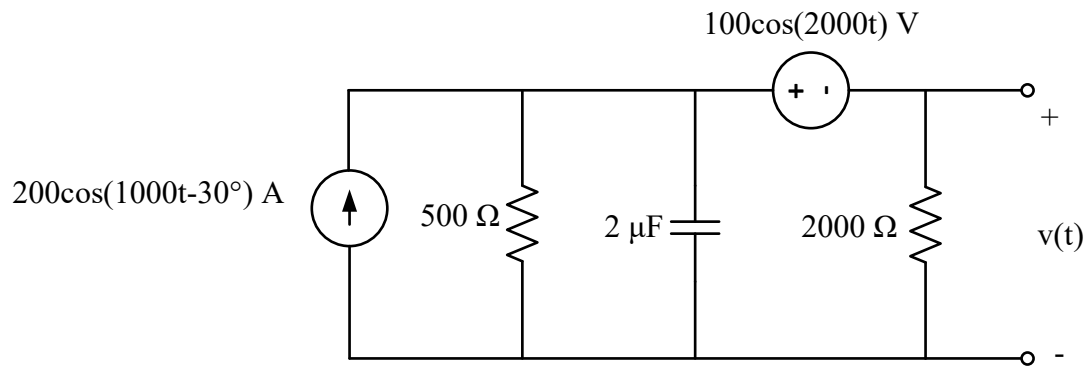(5) For the following circuit, determine  $v(t)$  using superposition.



$v(t) =$  \_\_\_\_\_

- (6) A single-phase load draws  $70 \text{ A}_{\text{rms}}$  at a power factor of 0.60 lagging from a  $240\text{-V}_{\text{rms}}$  60-Hz power line. To reduce the effective current drawn from the power line, a capacitance is placed in parallel with the load.
- Find the value of capacitance necessary to increase the power factor of the load to 0.98 lagging. (15 pts.)
  - Find the RMS current drawn from the line after the capacitance found in part a is placed in parallel with the load. (5 pts.)
  - What should the power factor be corrected to so that the minimum current is drawn? (5 pts.)

$$C = \underline{\hspace{10em}}$$

$$I_{\text{rms}} = \underline{\hspace{10em}}$$

$$\text{PF} = \underline{\hspace{10em}}$$

Name \_\_\_\_\_

(7) Two parallel single-phase loads are supplied by a 60-Hz, 208-V<sub>rms</sub> sinusoidal source.

Load 1 absorbs 300 W at a power factor of 0.70 leading

Load 2 absorbs 450 VA at a power factor of 0.80. lagging.

- Calculate the total complex power supplied by the source. (9 pts.)
- Calculate the power factor of the combined loads. Include whether it is leading or lagging. (2 pts.)
- Sketch and label the power triangle for Load 1. (7 pts.)
- Calculate the impedance of Load 2. (7 pts.)

$S_{\text{total}} =$  \_\_\_\_\_

$\text{PF}_{\text{total}} =$  \_\_\_\_\_


$Z_2 =$  \_\_\_\_\_

Power Triangle (Load 1)
-------------------------

Problem Score / 25
-----------------------




(8) For the circuit below,

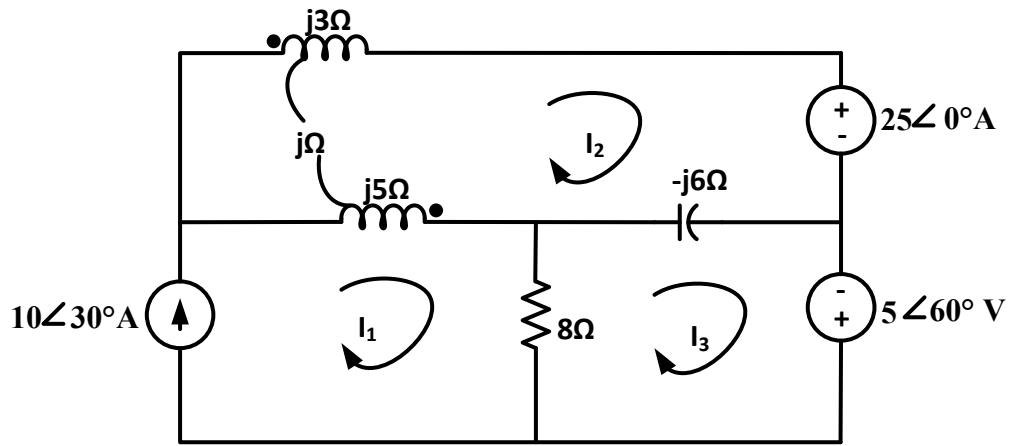

Write a set of mesh current equations in the matrix form. Do not solve. (25 pts)

$$\begin{bmatrix} \phantom{0} \\ \phantom{0} \\ \phantom{0} \end{bmatrix} = \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} \phantom{0} \\ \phantom{0} \\ \phantom{0} \end{bmatrix}$$

(9) For the circuit below,

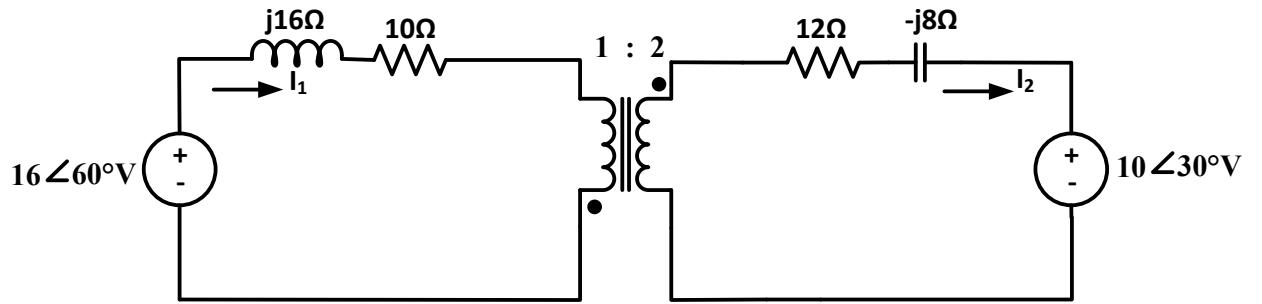


Find the currents  $I_1$  and  $I_2$ . (Keep your answer in the polar form) (25 pts)

$$I_1 = \underline{\hspace{10em}}$$

$$I_2 = \underline{\hspace{10em}}$$

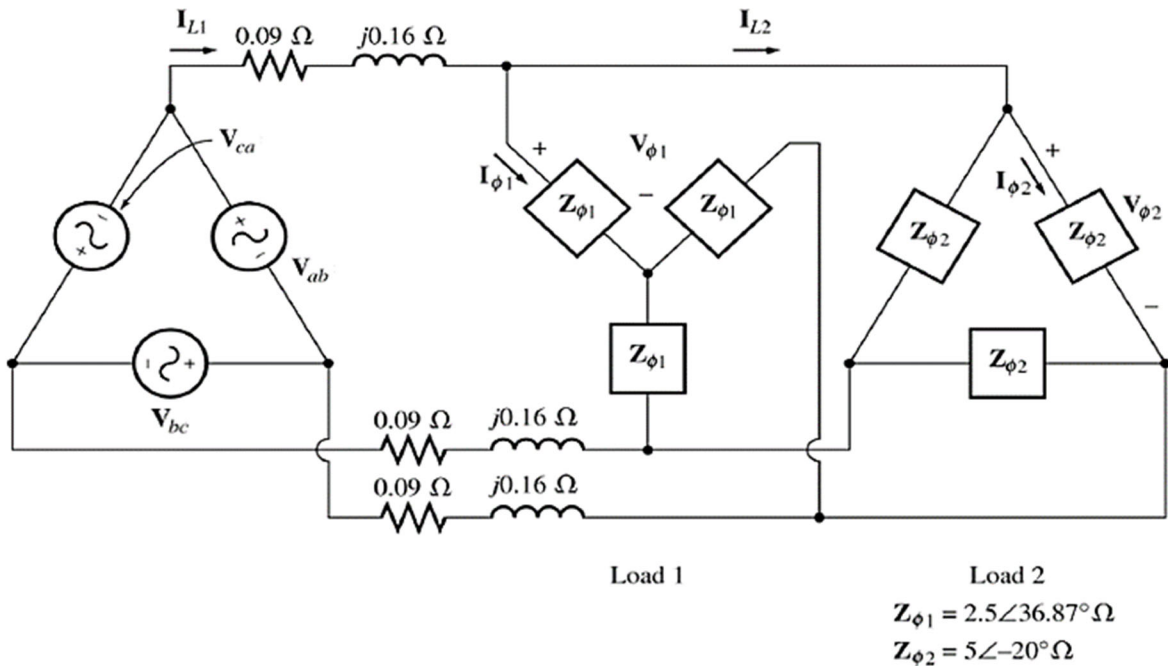(10) A three-phase power system shown below has two loads. The  $\Delta$ -connected source is producing a line-to-line voltage of 480V and the line impedance is  $(0.09+j0.16)\ \Omega$ . Load 1 is Y-connected with an impedance of  $2.5\angle 36.87^\circ\ \Omega$  and load 2 is  $\Delta$ -connected with an impedance of  $5\angle -20^\circ\ \Omega$ .



- a. Draw the per-phase equivalent circuit with correct values of all components. Take phase A line-to-neutral voltage to be your angle reference. **(5 points)**
  
- b. What is the magnitude of the line-to-line voltage of the two loads? **(5 points)**
  
- c. What is the magnitude of the line Current,  $I_{L1}$ ? **(5 points)**
  
- d. Find the **real** and **reactive** powers supplied to each load. **(10 points)**